

**Chandigarh Engineering College Landran, Mohali**  
Department of Applied Sciences

**Assignment No 1**

**Max Marks: 10**

**Subject and Subject code:** BEE (BTEE-101-18)

**Semester:** I<sup>st</sup>

**Date on which assignment given:**

**Date of submission of assignment :**

**Course Outcomes: Student will be able to**

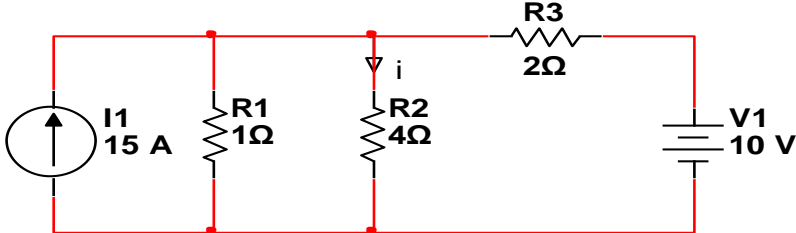
CO1: differentiate circuits based on their composition, terminology and their mathematical analysis.

CO2: analyze the behavior of electrical circuits based on alternating currents as their power supply; solve AC circuits and their mathematical analysis.

CO3: understand the basic magnetic circuit; construction as well as working principle of transformer.


CO4: study the working principles of various electrical machines such as three- phase induction motor, single phase induction motor, dc motor and synchronous generator.

CO5: understand the components of low voltage electrical installations.

Assignment related to COs		Relevance to CO No.
Q1.	(i) There are two wires A & B of same material. A is 10 times longer than B and has one fifth of the cross-section as that of B. If the resistance of A is 1 ohm. What is the resistance of B? (2 marks)  (ii) State Superposition theorem. (2 marks)	CO-1
Q2.	Using the Nodal Analysis, determine the current through $4\Omega$ resistor and find the power dissipated by $4\Omega$ resistor in fig. (3 marks) 	CO-1

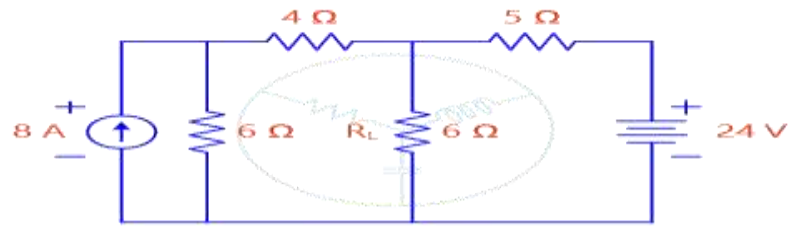Q3.

Calculate the current through  $6\Omega$  load resistor using thevenin's theorem and verify the result with Norton's theorem. (3 Marks)



CO-1