

# NETWORK THEOREMS

## CONTENTS:

- Norton's Theorem
- Thevenin's Theorem
- Solving Electrical circuits

Er. Ripple Sahni

Assistant Professor

Chandigarh Engineering College

Landran, Mohali

## WHY NETWORK THEOREMS??


- Network theorems are used to reduce complicated networks to simpler less-complicated networks
- Electric circuit theorems are always beneficial to help find voltage and currents in multi-loop circuits. These theorems use fundamental rules or formulas and basic equations of mathematics to analyze basic components of electrical or electronics parameters such as voltages, currents, resistance, and so on.
- These fundamental theorems include the basic theorems like Superposition theorem, Norton's theorem and Thevenin's theorems.

## NORTON'S THEOREM

- A linear active network consisting of the independent or dependent voltage source and current sources and the various circuit elements can be substituted by an equivalent circuit consisting of a current source in parallel with a resistance.
- The Norton's theorems reduce the networks equivalent to the circuit having one current source, parallel resistance and load. Norton's theorem is the converse of Thevenin's Theorem. It consists of the equivalent current source instead of an equivalent voltage source as in Thevenin's theorem.

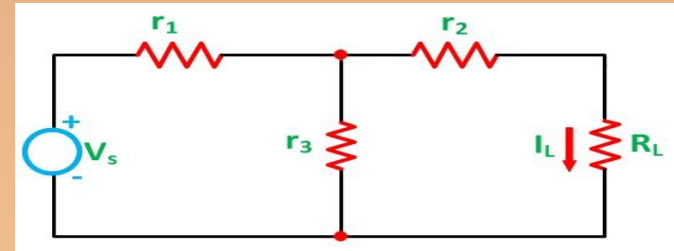
# EXPLANATION OF NORTON'S THEOREM

- In order to find the current through the load resistance  $R_L$  as shown in the circuit diagram below



**Step 1:-** Norton's equivalent circuit is drawn by keeping the equivalent resistance  $R_{eq}$  in parallel with the short circuit current  $I_{sc}$ .
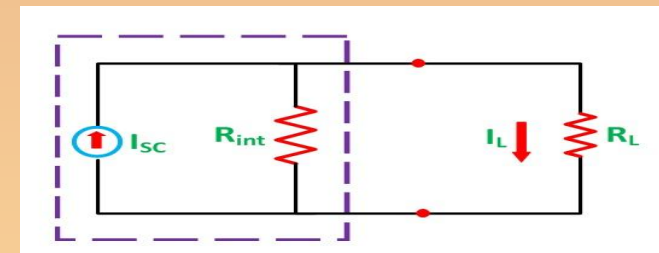
$$I_L = I_{sc} \frac{R_{eq}}{R_{eq} + R_L}$$




where,  $I_L$  is the load current,  $I_{sc}$  is the short circuit current

$R_{eq}$  is the equivalent resistance of the circuit,  $R_L$  is the load resistance of the circuit
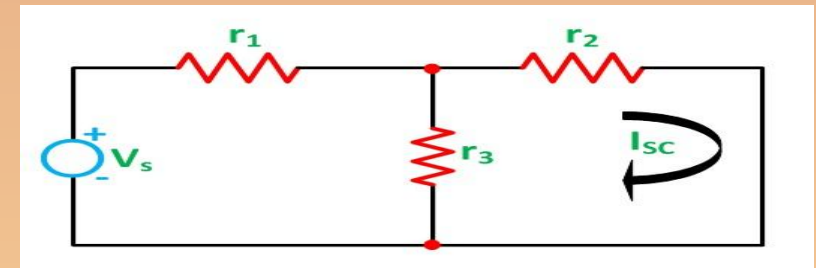
# EXPLANATION OF NORTON'S THEOREM

**Step 2** – In order to find  $I_{SC}$ , short the load terminals and find the short circuit current  $I_{SC}$  flowing through the shorted load terminals using conventional network analysis methods.



Now, the value of current  $I$  flowing in the circuit is found out by the equation

$$I = \frac{V_s}{r_1 + \frac{r_2 r_3}{r_2 + r_3}}$$

and the short-circuit current  $I_{SC}$  is given by the equation shown below:


$$I_{sc} = I \frac{r_3}{r_3 + r_2}$$

## EXPLANATION OF NORTON'S THEOREM

**Step 3** – Find the internal resistance  $R_{eq}$  of the source network by deactivating the constant sources as shown in the circuit diagram below and the value of the equivalent resistance is calculated by:

$$R_{eq} = r_1 \parallel r_3 + r_2$$
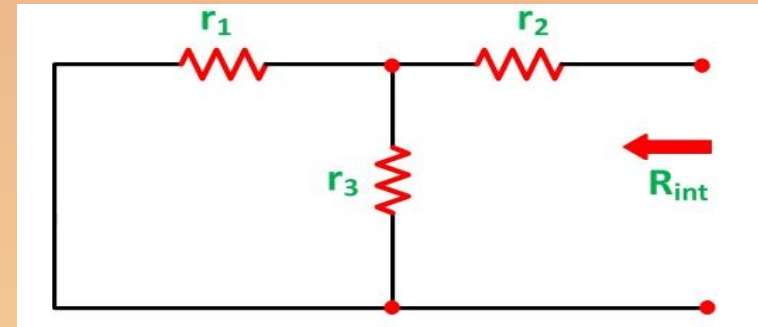
$$R_{eq} = \frac{r_1 r_3}{r_1 + r_3} + r_2$$



**Step 4** – Reconnect the load resistance  $R_L$  of the circuit across the load terminals and find the current through it known as load current  $I_L$ .


$$I_L = I_{SC} \frac{R_{eq}}{R_{eq} + R_L}$$

## THEVENIN'S THEOREM

- A linear active network consisting of the independent or dependent voltage source and current sources and the various circuit elements can be substituted by an equivalent circuit containing a single source and a single resistor.
- Thevenin's theorem implies that we can replace arbitrarily complicated networks with simple networks for purposes of analysis
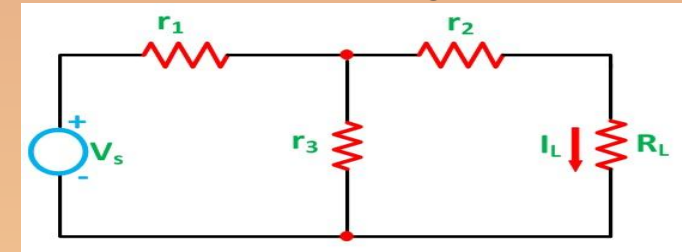
## EXPLANATION OF THEVENIN'S THEOREM


In order to find the current through the load resistance  $R_L$  as shown in the circuit diagram below



**Step 1:-** Thevenin's equivalent circuit is drawn by keeping the equivalent resistance  $R_{th}$  in series with Thevenin Voltage  $V_{th}$ .

The load current  $I_L$  is given as:

$$I_L = \frac{V_{TH}}{R_{TH} + r_L}$$

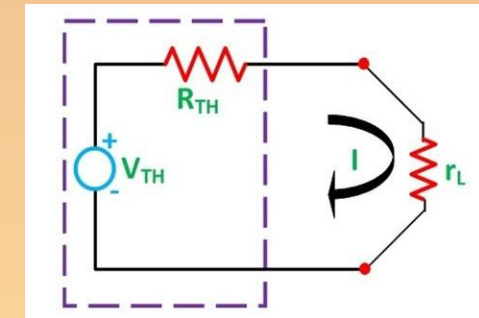

$V_{TH}$  is the Thevenin's equivalent voltage

$R_{TH}$  is the Thevenin's equivalent resistance

$r_L$  is the **load resistance**




# EXPLANATION OF THEVENIN'S THEOREM
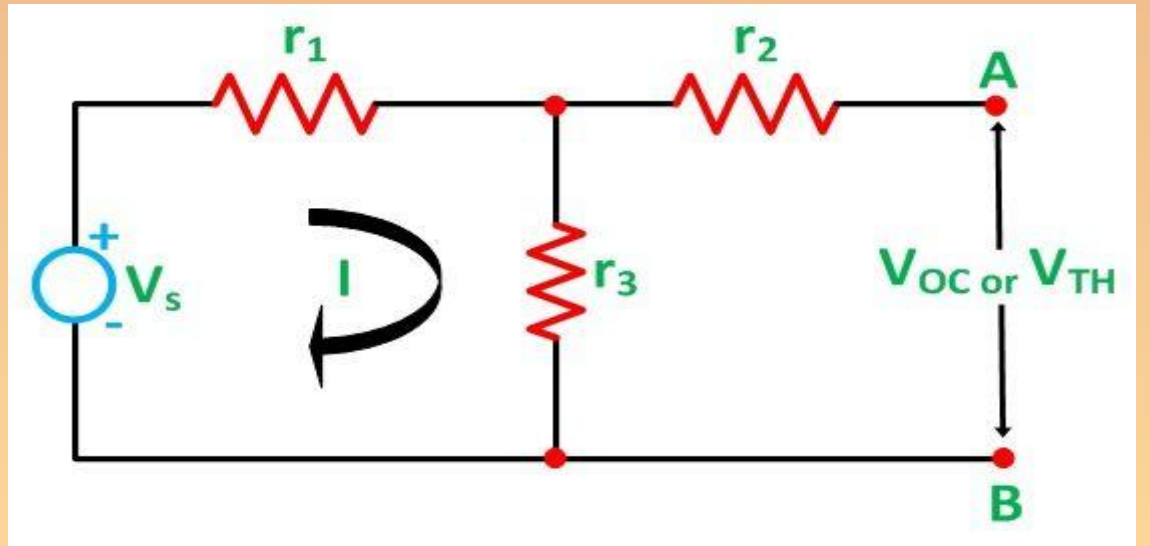
## Step 2:

In order to find  $V_{TH}$ , open the load terminals from the circuit as shown in the figure below and  $V_{OC}$  or  $V_{TH}$  is calculated.

$$V_{OC} = I r_3 = \frac{V_s}{r_1 + r_3} r_3$$




# EXPLANATION OF THEVENIN'S THEOREM

**Step 3** – Find the equivalent resistance  $R_{eq}$  of the source network by deactivating the constant sources as shown in the circuit diagram below and the value of the equivalent resistance is calculated by:

$$R_{eq} = r_1 \parallel r_3 + r_2$$
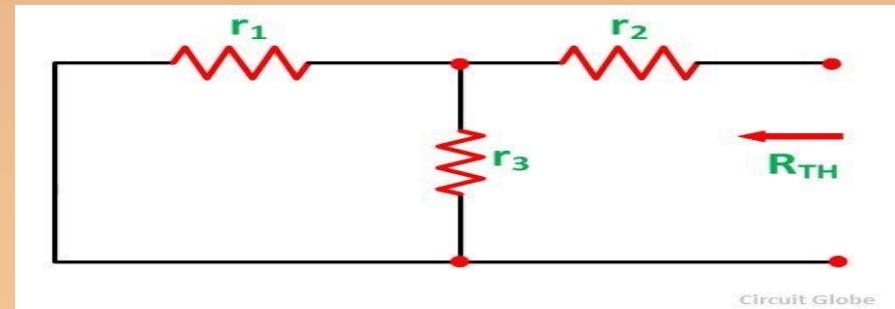
$$R_{eq} = \frac{r_1 r_3}{r_1 + r_3} + r_2$$




**Step 4** – Reconnect the load resistance  $R_L$  of the circuit across the load terminals and find the current through it known as load current  $I_L$ .

$$I_L = \frac{V_{TH}}{R_{TH} + r_L}$$

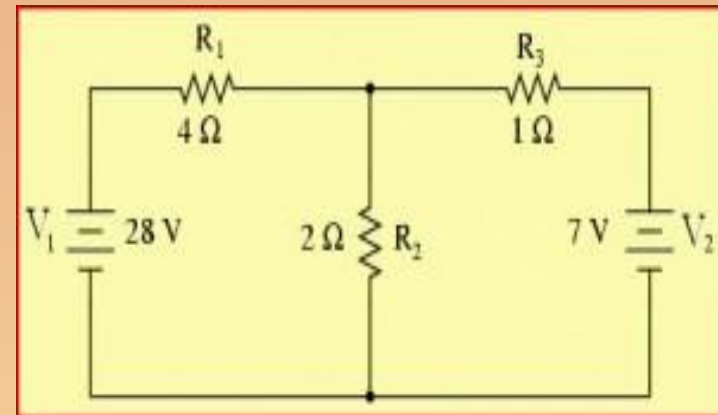
## PROBLEMS RELATED TO THEOREMS

- Find the current in  $2\Omega$  resistor using Norton's Theorem



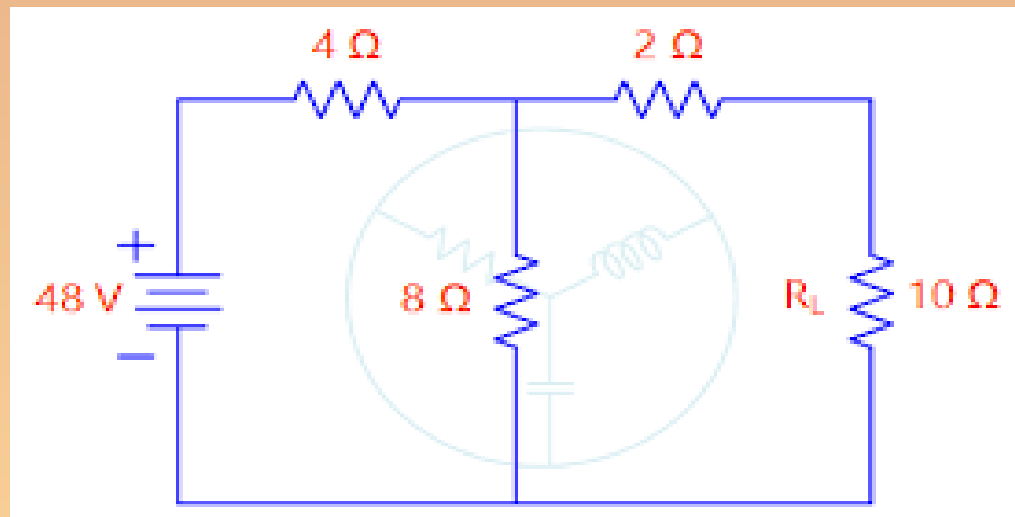
## PROBLEMS RELATED TO THEOREMS

- Find the current in  $10\Omega$  resistor using Thevenin's Theorem


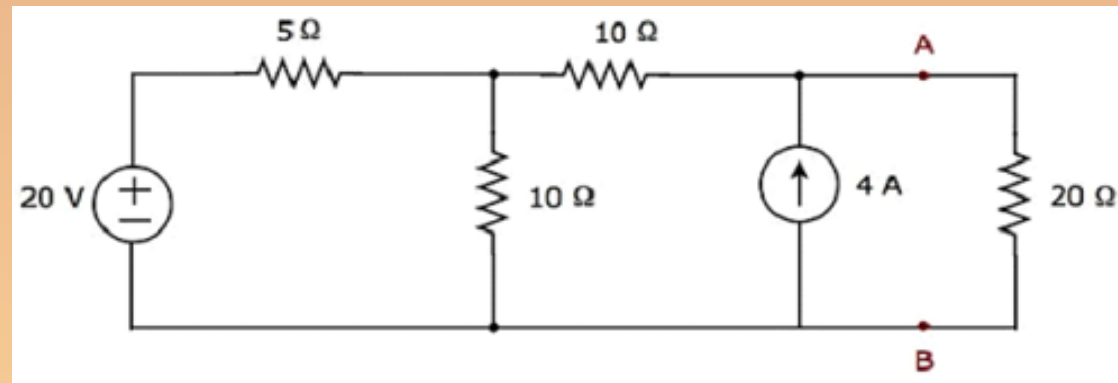
## PROBLEMS RELATED TO THEOREMS

- Find the current in  $20\Omega$  resistor using Thevenin's Theorem



THANKS