


# AC FUNDAMENTALS

# Contents

- Alternating Current
  - Sinusoidal Alternating Quantity
  - Average and RMS Value
  - Peak and Form Factor
- AC Circuit
  - Purely resistive circuit
  - Purely inductive circuit
  - Purely capacitive circuit
- AC Series Circuits
  - R-L Series Circuit
  - R-C Series Circuit
  - R-L –C Series Circuit
- Resonance
  - Resonance In Series
  - Resonance Frequency
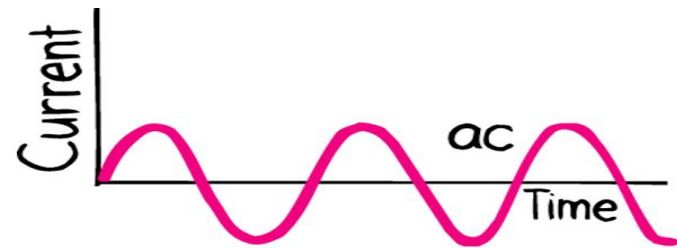
# What is A.C. and D.C.

- In Alternating current, movement of electric charge periodically reverses its direction.



- Whereas in DC, flow of electric charge is only in one direction.




## Why we use A.C. in homes

- AC voltage is capable of converting voltage levels just with use of transformers.
  - To transmit AC over a long distance, voltage is stepped up to 400 KV at generating stations and stepped down at a low level , 400/230 V for household and commercial utilization.
- AC motors are simple in construction, more efficient and robust as compared to DC motors
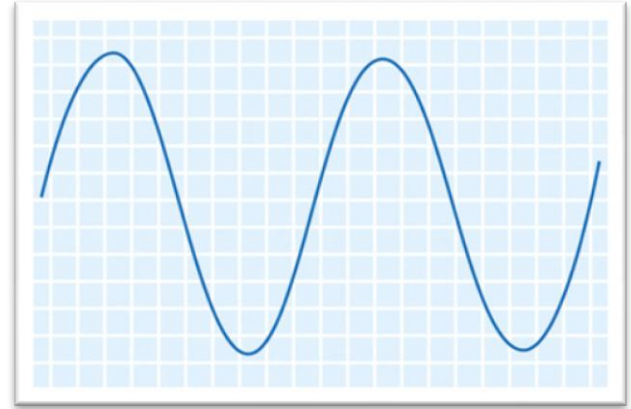
# Sinusoidal Alternating Quantity

Alternating quantity that varies according to sin of angle  $\theta$ .



The instantaneous value of a sine-wave voltage for any angle of rotation is expressed in the formula:

$$V = V_m \sin \theta$$


$\theta$  is the angle

$V_m$  = the maximum voltage value

$V$  = the instantaneous value of voltage at angle  $\theta$ .

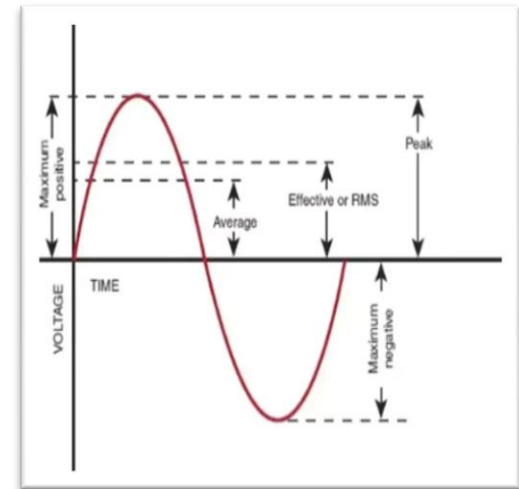
# Terms to know

- **Cycle**
  - When an Alternating qty goes through complete set of positive and negative values
  - Goes through 360 electrical degrees.
- **Alternation**
  - One half cycle
- **Time Period**
  - Time taken to complete one cycle by AC.
- **Frequency**
  - No of cycle made per second.
- **Amplitude**
  - Maximum value attained by an alternating quantity in one cycle
  - Also called Peak Value / Max. Value


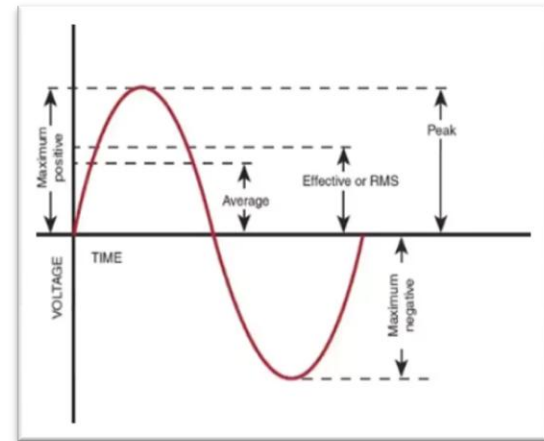
# Expressing Alternating Quantities

- In AC system, alternating current and voltage varies from instant to instant.
- Three ways to express
  - Peak Value
  - Average Value
  - RMS value



# Average Value

- Average value of whole sinusoidal waveform over one complete cycle is zero as two halves cancel each other out.
  - So average value is taken over half a cycle and taken as 0.637 times peak value.

The alternating current varying sinusoidally is given by

$$I = I_m \sin \theta$$

Consider an elementary strip of thickness  $d\theta$  in the + ive half cycle,  $i$  be its mid ordinates.

Thus, Area of strip =  $i d\theta$

$$\text{Area of half cycle} = \int_0^{\pi} i d\theta = \int_0^{\pi} I_m \sin \theta d\theta$$


$$= I_m (-\cos\theta)_0^{\pi}$$

$$= I_m \{-(\cos\pi - \cos 0)\}$$

$$= 2I_m$$

$$\text{Average Value } I_{av} = \frac{\text{Area of alternation}}{\text{Base}}$$


$$= \frac{2I_m}{\pi} = 0.637 I_m$$

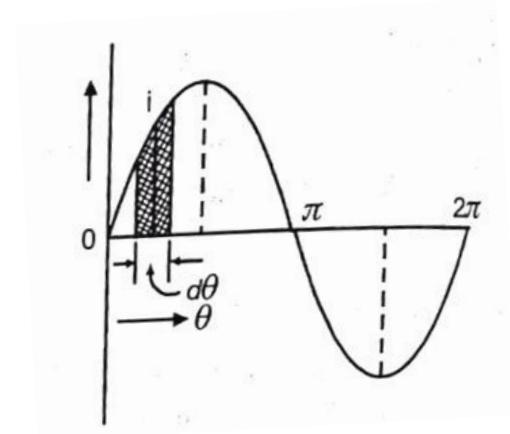


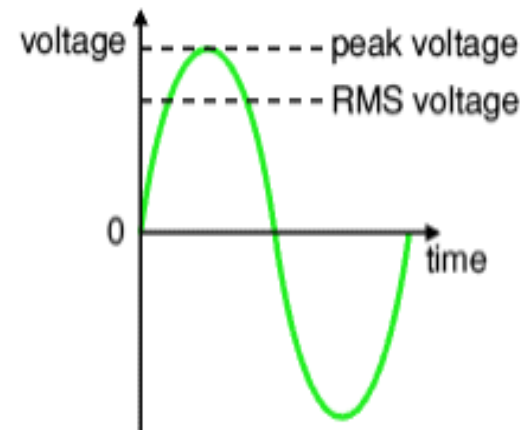
# R.M.S. Value

- Root mean square value is effective value of varying voltage or current.
  - It is equivalent steady DC value that gives the same effect.
- Two methods of finding RMS value
  - Graphical Method
  - Analytical Method



# R.M.S. Value

An alternating current is given by

$$i = I_m \sin\theta$$

$$\text{Area of strip} = i^2 d\theta$$

Area of squared wave in first half cycle

$$\int_0^\pi i^2 d\theta = \int_0^\pi (I_m \sin\theta)^2 d\theta$$

$$= I_m^2 \int_0^\pi \sin^2\theta \cdot d\theta = I_m^2 \int_0^\pi \left( \frac{1 - \cos 2\theta}{2} \right) d\theta$$

$$= \frac{1}{2} I_m^2 \int_0^\pi (1 - \cos 2\theta) \cdot d\theta = \frac{1}{2} I_m^2 \left( \theta - \frac{\sin 2\theta}{2} \right) \Big|_0^\pi$$


$$= \frac{1}{2} I_m^2 \left\{ (\pi - 0) - \frac{\sin 2\pi - \sin 0}{2} \right\}$$

$$= \frac{1}{2} I_m^2 \{ (\pi - 0) - (0 - 0) \}$$


$$= \frac{\pi}{2} I_m^2$$

$$\text{R.M.S. value } I_{rms} = \sqrt{\frac{\text{Area of first half of squared wave}}{\text{Base}}}$$
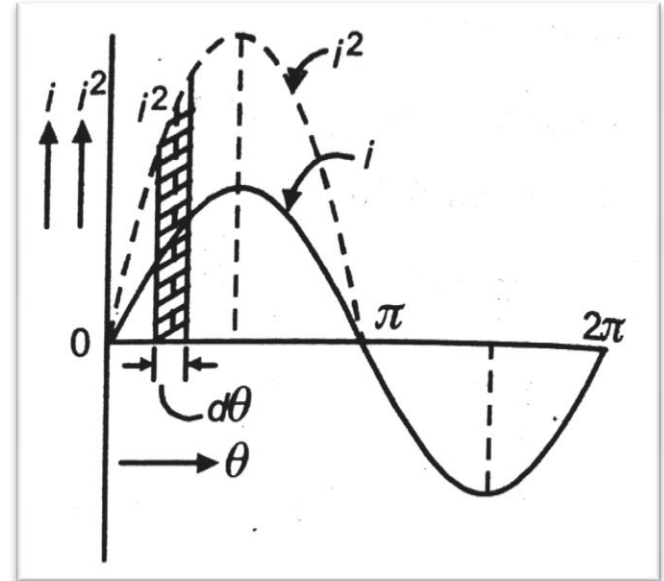
$$= \sqrt{\frac{\pi I_m^2}{2\pi}} = \sqrt{\frac{I_m^2}{2}} = 0.707 I_m$$



# R.M.S. Value of Half wave rectifier

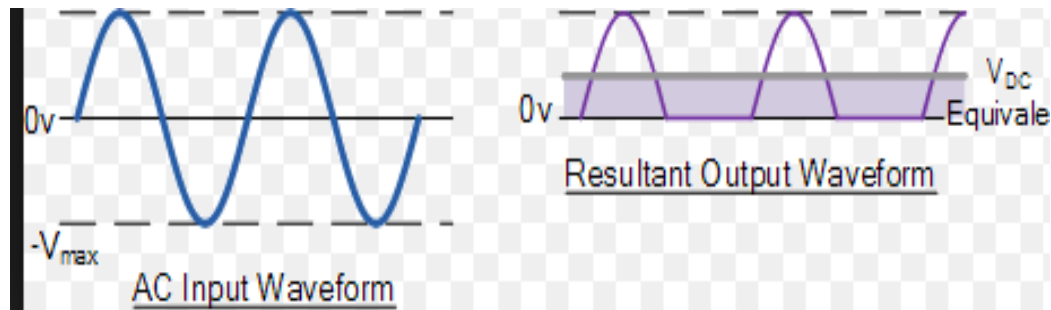

$$\therefore \text{rms current, } I = \sqrt{\frac{1}{2\pi} \int_0^{\pi} i^2 d\theta} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} I_m^2 \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta} = \sqrt{\frac{I_m^2}{4\pi} \left( \theta - \frac{\sin 2\theta}{2} \right)_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} (\pi)} = \frac{I_m}{2} = 0.5 I_m$$

$$\therefore I = 0.5 I_m \text{ for a half wave rectified a.c.}$$

## Peak Factor

- Ratio of the Maximum value to the R.M.S. value of an alternating quantity

It is denoted by

$$K = \frac{\text{Maximum Value}}{\text{RMS Value}}$$

Where  $K = 1.414$

- Peak factor is also called the crest factor or amplitude factor.

## Form Factor

Form Factor is ratio of R.M.S. value to the average value of an alternating quantity. It is denoted by  $K_f$

$$K_f = \frac{\text{R.M.S. Value}}{\text{Average Value}}$$

Where  $K_f = 1.11$

## Question For Practice

Q: An alternating voltage is given by  $V = 282.8 \sin 377t$ .

Find

(i) Frequency

(ii) RMS value

(iii) Average value

(iv) instantaneous value of voltage when  $t$  is 3 m sec.

## A.C. Circuit

- Circuits in which currents and voltages vary sinusoidally, ie vary with time are called A.C. circuits.
  - All A.C. circuits are made up of combination of resistance  $R$ , inductance  $L$  and capacitance  $C$ .
  - The circuit elements  $R, L$  and  $C$  are called circuit parameters.
- To study a general A.C. circuit it is necessary to consider the effect of each separately.

# Purely Resistive Circuit

- In purely resistive circuits, all the power is dissipated by resistors.
  - Voltage and current in same phase.


$$V = V_m \sin \omega t \dots (1)$$

$$I = \frac{V}{R} = V_m \frac{\sin \omega t}{R} \quad (\text{Using Ohm's Law})$$

At  $\omega t = 90^\circ$ ,  $\sin \omega t = 1$  & current will be maximum.

$$I_m = \frac{V_m}{R}$$

$$I = I_m \sin \omega t \dots (2)$$

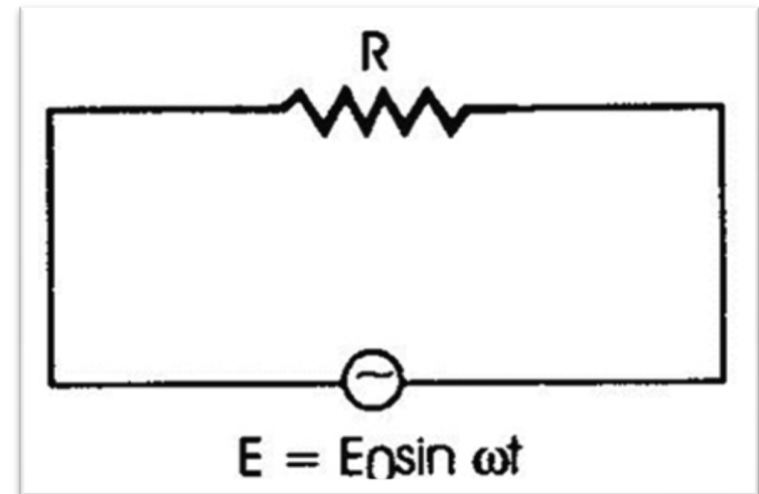

For purely resistive circuits, the voltage and current are in phase with each other.




# Phasor and Wave Diagram of Purely Resistive Circuit

Average power consumed over a complete cycle

$$P = V_{\text{rms}} I_{\text{rms}}$$

$$P = VI$$

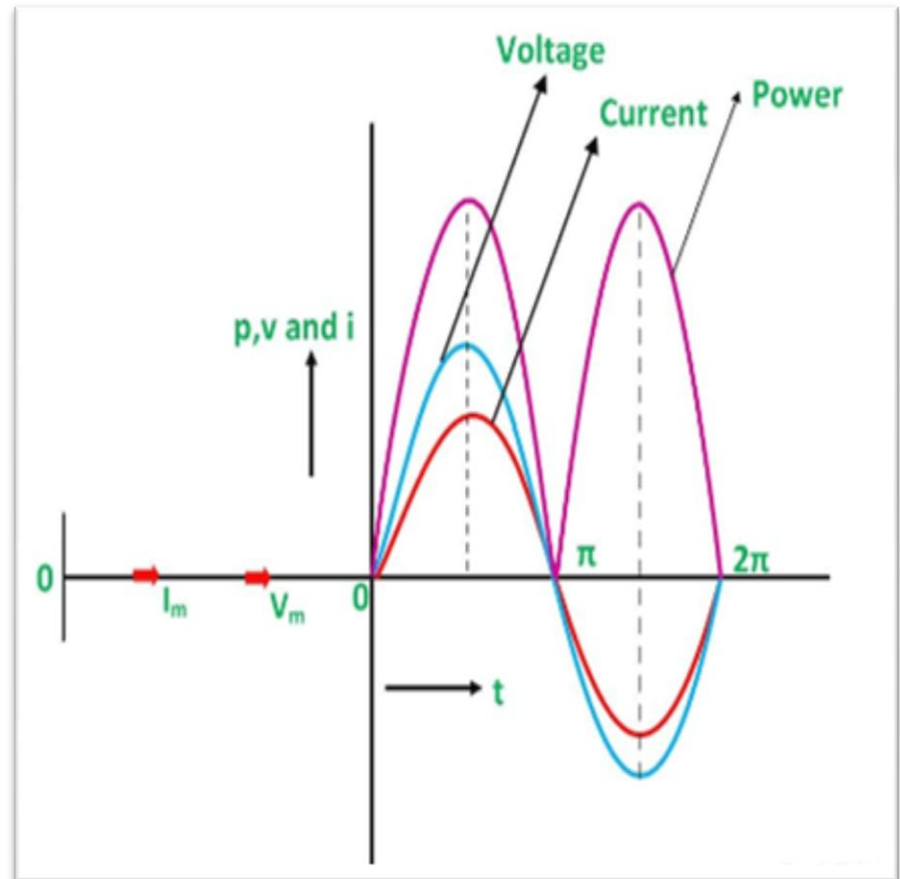

# Purely Inductive Circuit

- In purely inductive circuits, current lags the voltage by an angle of  $90^\circ$ 
  - No power consumed in pure inductive circuit

The alternating voltage is

$$V = V_m \sin \omega t$$

An alternating current  $i$  flows through the inductance which induces an emf in it, given by

$$e = -L \frac{di}{dt}$$

This induced emf is equal and opposite of the applied voltage

$$V = -e = -(-L \frac{di}{dt})$$

$$V = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{V_m \sin \omega t}{L} dt$$

$$\int di = \int \frac{V_m \sin \omega t}{L} dt$$

$$i = \frac{V_m}{\omega L} (-\cos \omega t)$$


$$i = \frac{V_m}{\omega L} \sin (\omega t - 90^\circ)$$

$$i = \frac{V_m}{XL} \sin (\omega t - 90^\circ)$$

when  $\sin (\omega t - 90^\circ) = 1$ , value of current is maximum

$$I_m = \frac{V_m}{XL}$$

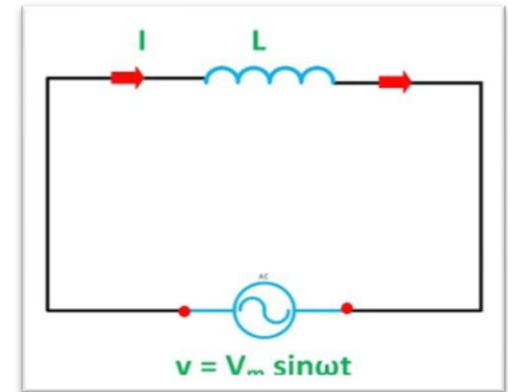
Therefore  $i = I_m \sin (\omega t - 90^\circ)$



# Phasor and Wave Diagram of Purely Inductive Circuit

Average power consumed over a complete cycle

$P = \text{zero}$

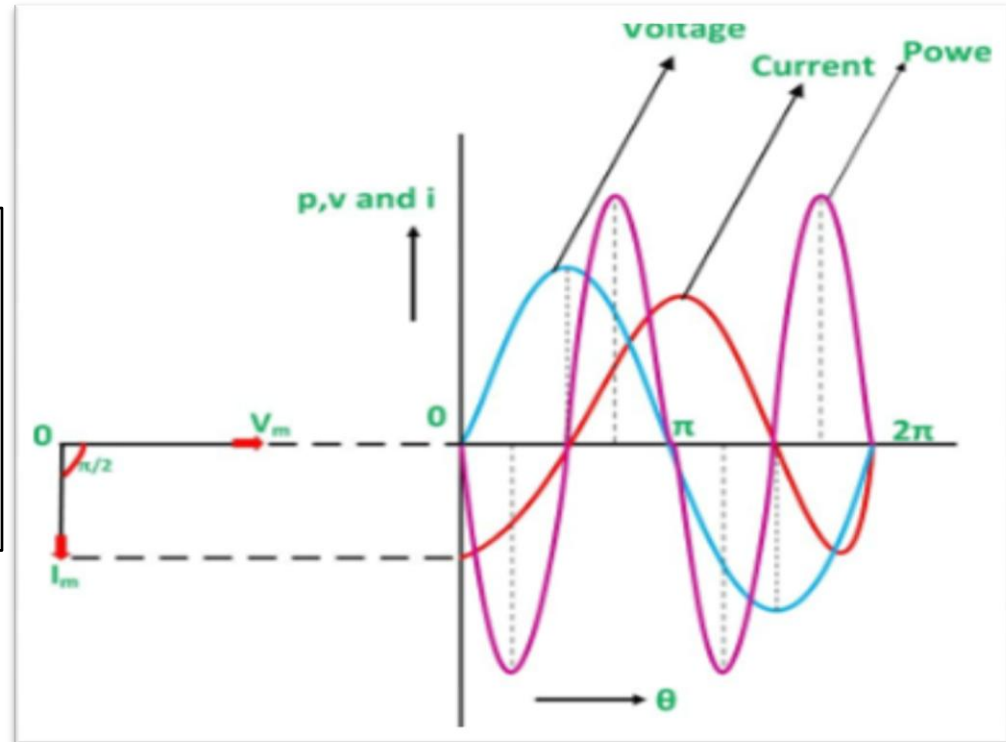

# Purely Capacitive Circuit

- In purely capacitive circuits, current leads the voltage by an angle of  $90^\circ$ 
  - No power consumed in pure capacitive circuit

$$V = V_m \sin \omega t \dots\dots(1)$$

The current in the circuit at any instant is

$$i = dq/dt$$

$$i = d(CV)/dt = C dV/dt = C d(V_m \sin \omega t)/dt$$

$$i = \omega CV_m \cos \omega t = \omega CV_m \sin (\omega t + 90^\circ)$$

$$i = \frac{V_m}{1/\omega C} \sin (\omega t + 90^\circ)$$

$$i = \frac{V_m}{X_C} \sin (\omega t + 90^\circ) \dots\dots\dots (2)$$


At  $\sin (\omega t + 90^\circ) = 1$ , value of current will be maximum

i.e.  $I_m = \frac{V_m}{X_C}$  , substituting in eqn(2)

$$i = I_m \sin (\omega t + 90^\circ) \dots\dots\dots (3)$$

By comparing eqn (1) and (3),

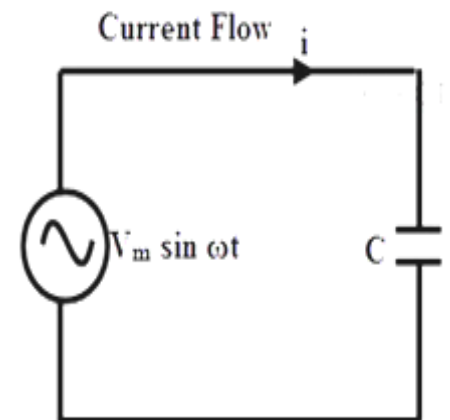
Current leads the voltage by an angle of  $90^\circ$



# Phasor and Wave Diagram of Purely Capacitive Circuit

Average power consumed over a complete cycle

$P = \text{zero}$

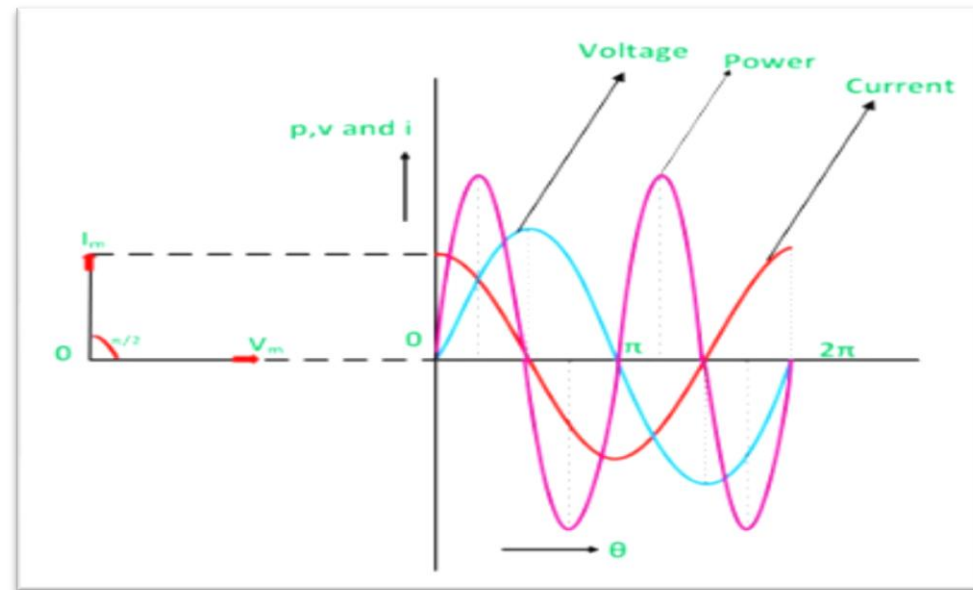

## A.C. Series Circuit

- In actual practice, A.C. circuit contain two or more than two components (R,L,C) connected in series or parallel.
  - Three types of A.C. series circuits
    - R-L series circuit
    - R-C series circuit
    - R-L-C series circuit

# R-L Series Circuit

This circuit contains a resistance  $R$  and an inductance  $L$  in series

Let  $V$  = supply voltage

$I$  = circuit current

$V_R$  = voltage drop across  $R = IR$


$V_L$  = voltage drop across  $L = IX_L = 2\pi fLI$

$\Phi_L$  = phase angle between  $I$  and  $V$

Since  $I$  is common to both elements  $R$  and  $L$ , this is used as reference phasor.

The voltage  $V_R$  is in phase with  $I$  and  $V_L$  leads  $I$  by  $90^\circ$ .

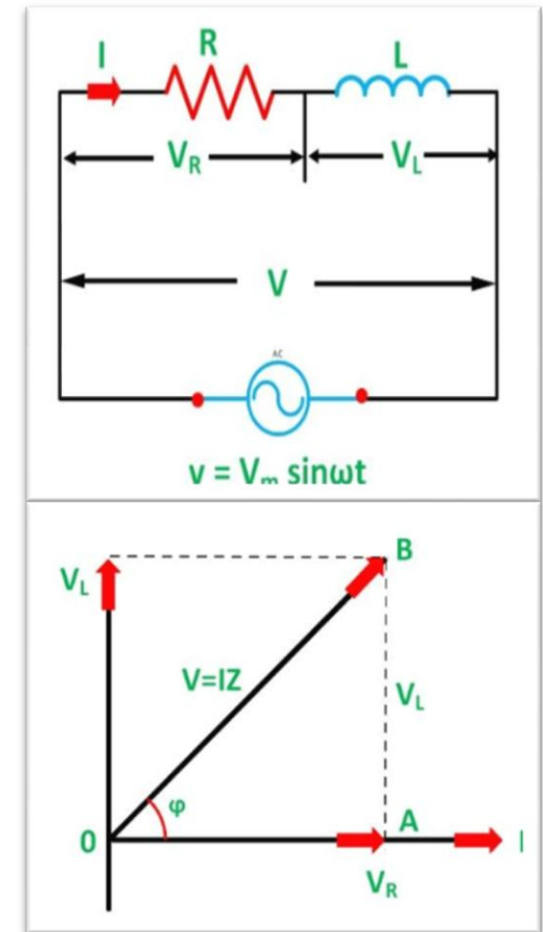The voltage  $V$  is the phasor sum of  $V_R$  and  $V_L$



# Phasor Diagram of R-L Series Circuit

The triangle having  $V_R$ ,  $V_L$  and  $V$  as its sides is called voltage triangle for a series R-L circuit.

The phase angle  $\Phi_L$  between the supply voltage  $V$  and the circuit current  $I$  is the angle between the hypotenuse and the side  $V_R$ .

It is seen that the current  $I$  is lagging behind the voltage  $V$  in an R-L circuit.

$$V^2 = V_R^2 + V_L^2$$

$$V^2 = (RI)^2 + (X_L I)^2$$

$$V^2/I^2 = R^2 + X_L^2$$


$$V/I = \sqrt{R^2 + X_L^2}$$

$$Z_L = \sqrt{R^2 + X_L^2}$$

$Z_L$  is called the impedance of a series R-L circuit

$$Z_L = V/I$$

$$V = Z_L I$$

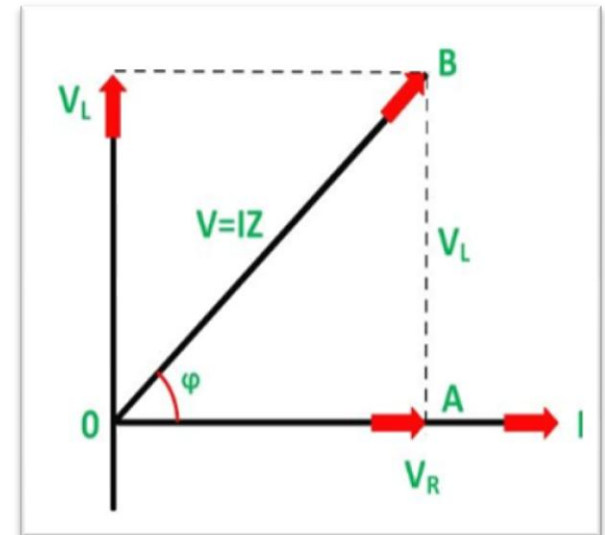



# Impedance Triangle For R-L Series Circuit


- If the length of each side of the voltage triangle is divided by current  $I$ , the impedance triangle is obtained.
  - The following results may be found from an impedance triangle for a series R-L circuit:

$$Z_L = \sqrt{R^2 + X_L^2}$$

$$R = Z_L \cos\Phi_L$$

$$X_L = Z_L \sin\Phi_L$$

$$\tan\Phi_L = X_L / R$$

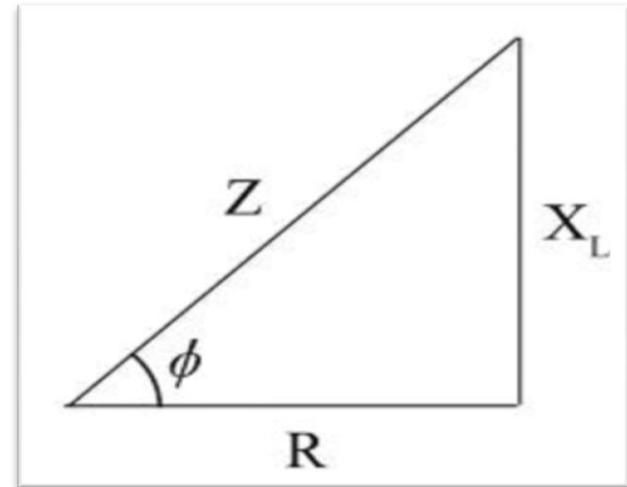


# Phasor and Wave Diagram of R-L Series Circuit

Average power consumed over a complete cycle

$$P = V_{\text{rms}} I_{\text{rms}} \cos\phi$$

$$P = V I \cos\phi$$

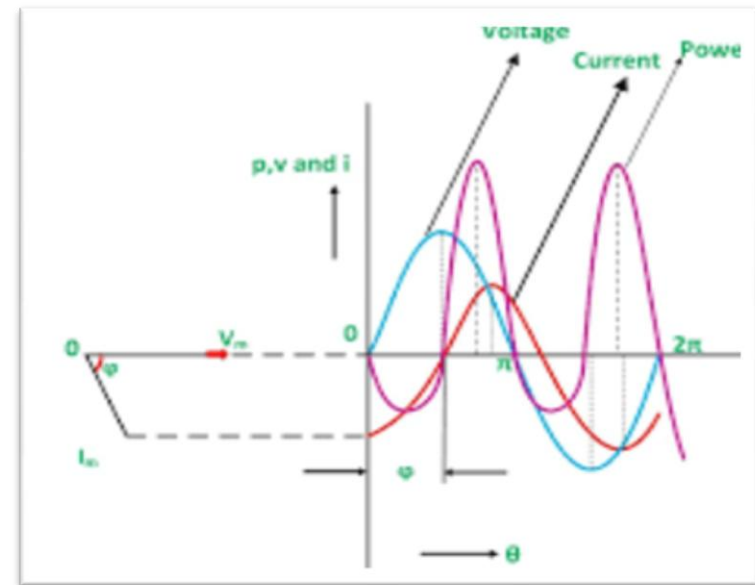

# R-C Series Circuit

This circuit contains a resistance  $R$  and a capacitance  $C$  in series

Let  $V$  = supply voltage

$I$  = circuit current


$V_R$  = voltage drop across  $R = IR$

$V_C$  = voltage drop across  $C = IX_C = I/2\pi fC$

$\Phi_C$  = phase angle between  $I$  and  $V$

The voltage  $V_R$  is in phase with  $I$  and  $V_C$  lags  $I$  by  $90^\circ$ .

The voltage sum is  $V = V_R + V_C$

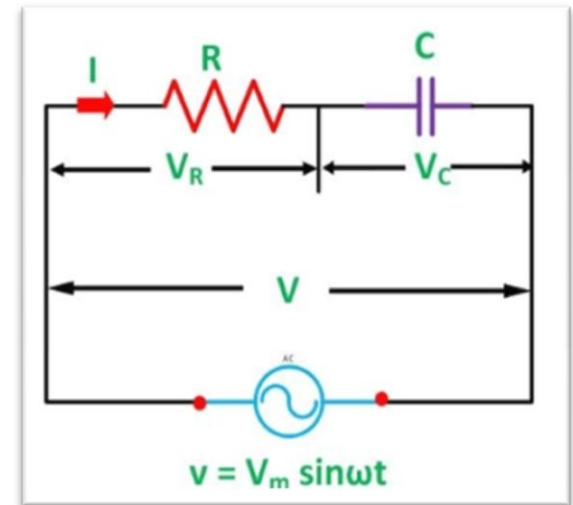

# Phasor Diagram of R-C Series Circuit

The triangle having  $V_R$ ,  $V_C$  and  $V$  as its sides is called voltage triangle for a series R-C circuit.

The phase angle  $\Phi_C$  between the supply voltage  $V$  and the circuit current  $I$  is the angle between the hypotenuse and the side  $V_R$ .

It is seen that the current  $I$  is leading behind the voltage  $V$  in an R-C circuit.

$$V^2 = V_R^2 + V_C^2$$

$$V^2 = (RI)^2 + (X_C I)^2$$

$$V^2 / I^2 = R^2 + X_C^2$$


$$V / I = \sqrt{R^2 + X_C^2}$$

$$Z_C = \sqrt{R^2 + X_C^2}$$

$Z_C$  is called the impedance of a series R-C circuit

$$Z_C = V / I$$

$$V = Z_C I$$

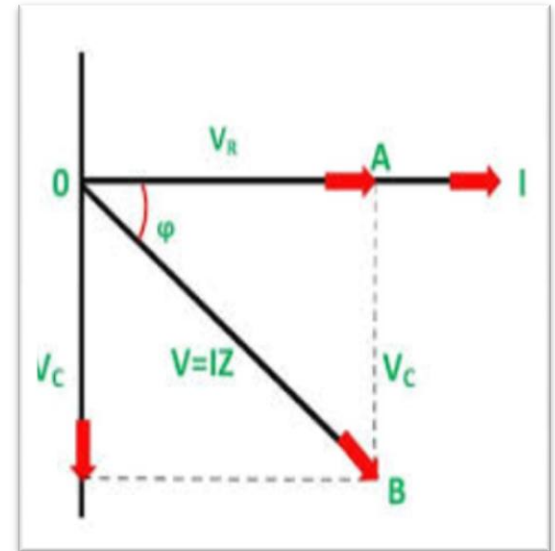

# Impedance Triangle For R-C Series Circuit


- If the length of each side of the voltage triangle is divided by current  $I$ , the impedance triangle is obtained.
  - The following results may be found from an impedance triangle for a series R-C circuit.

$$Z_c = \sqrt{R^2 + X_c^2}$$

$$R = Z_c \cos \Phi_c$$

$$X_c = Z_c \sin \Phi_c$$

$$\tan \Phi_c = X_c / R$$

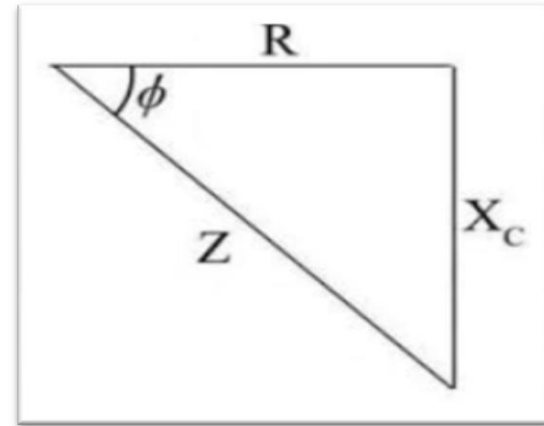


# Phasor and Wave Diagram of R-C Series Circuit

Average power consumed over a complete cycle

$$P = V_{\text{rms}} I_{\text{rms}} \cos\phi$$

$$P = V I \cos\phi$$

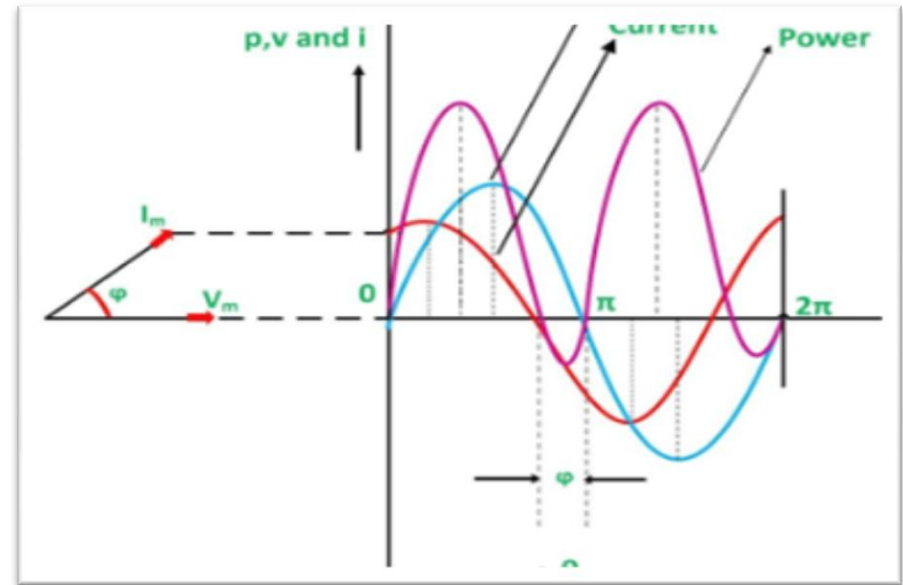

# R-L-C Series Circuit

- A circuit having R, L and C in series is called a R-L-C series circuit.
  - Current is used as reference phasor in series circuit since it is common to all the elements of circuit.


- There are four voltages

$V_R$  in phase with  $I$

$V_L$  leading  $I$  by  $90^\circ$


$V_C$  lagging  $I$  by  $90^\circ$

Total voltage  $V = V_R + V_L + V_C$

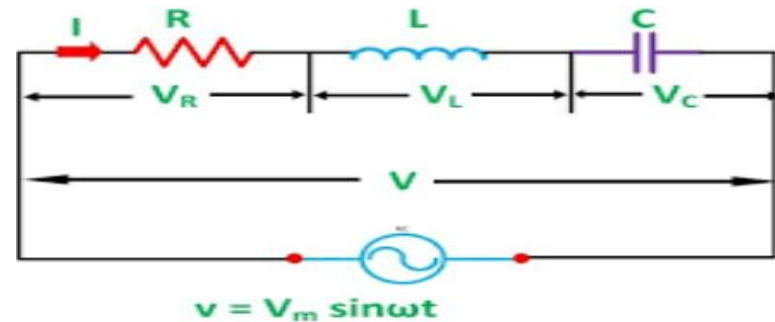
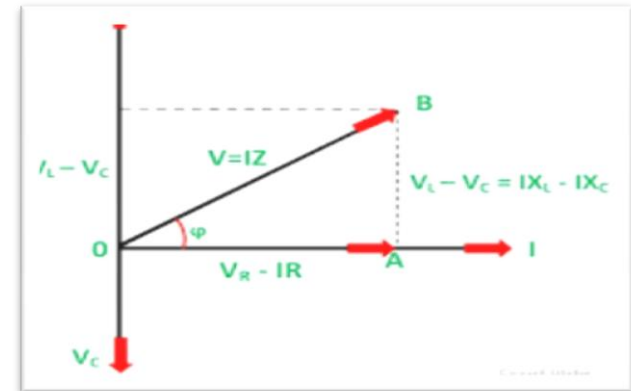
# Phasor Diagram of R-L-C Series Circuit

- $V_L$  and  $V_C$  are in opp. directions and their resultant is their arithmetic difference.
  - There are three possible cases in series RLC circuit
    - a)  $V_L < V_C$  i.e.  $X_L < X_C$
    - b)  $V_L > V_C$  i.e.  $X_L > X_C$
    - c)  $V_L = V_C$  i.e.  $X_L = X_C$





When  $X_L > X_C$ , the circuit is predominantly Inductive .  
Inductive circuits cause the current 'lag' the voltage.

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


When  $X_L < X_C$  the circuit is predominately Capacitive.  
Capacitive circuits cause the current to 'lead' the voltage.

$$V = I \sqrt{R^2 + (X_C - X_L)^2}$$


$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$
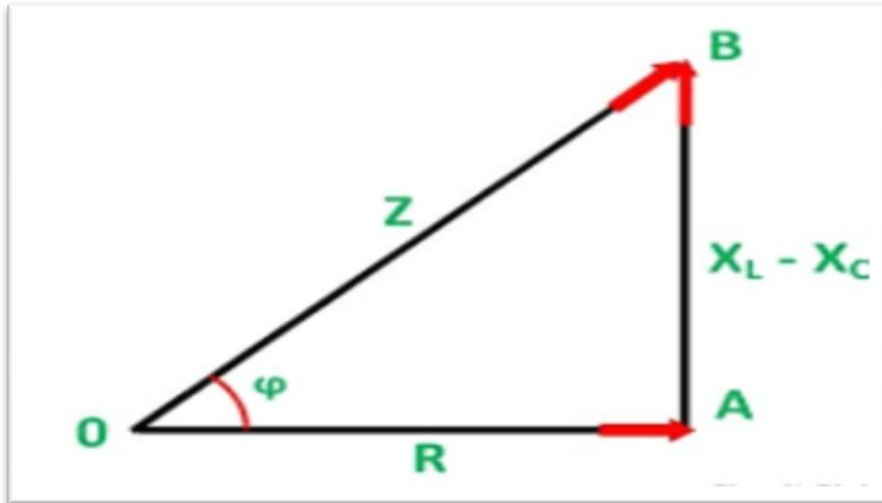
# Impedance Triangle For R-L-C Series Circuit

If the length of each side of a voltage triangle is divided by current  $I$ , the impedance triangle is obtained. The impedance triangle for series R-L-C circuit.



$$X_L > X_C$$

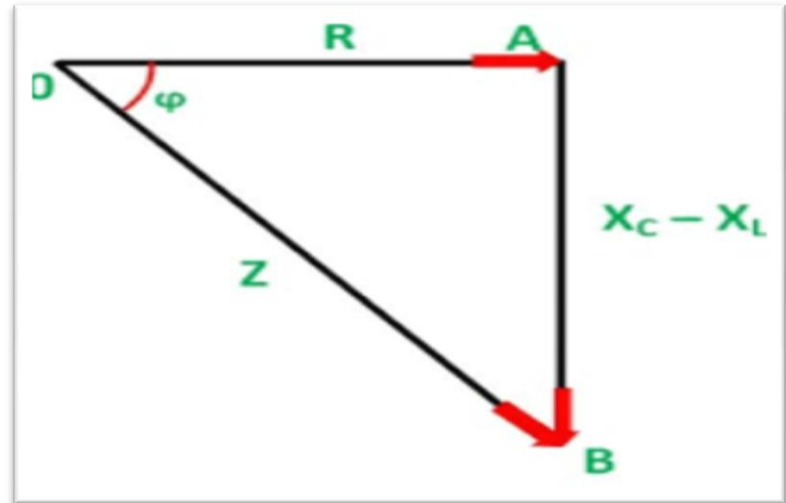

$$X_C > X_L$$

## Question For Practice


Q: A coil resistance  $10\ \Omega$  and inductance  $114.7\text{mH}$  is connected in series with capacitor of  $159.16\ \mu\text{F}$  across a  $200\text{V}$ ,  $50\ \text{Hz}$  supply.

Calculate

- (i) Inductive reactance
- (ii) Capacitive reactance
- (iii) Impedance
- (iv) Current
- (v) Voltage across coil and capacitor
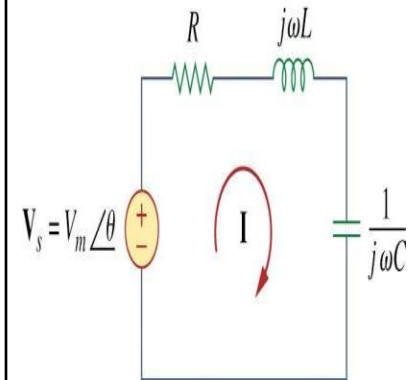
# Resonance

- Resonance is a condition in an RLC circuit in which the capacitive and inductive reactance are equal in magnitude, thereby resulting in a purely resistive impedance.
  - At resonance, the impedance consists only resistive component  $R$ .
  - The value of current will be maximum since the total impedance is minimum.
  - The voltage and current are in phase.
  - Maximum power occurs at resonance since the power factor is unity
  - Resonance circuits are useful for constructing filters and used in many application.



# Resonance Frequency


- Resonance frequency is the frequency where the condition of resonance occur.
  - Also known as center frequency.

$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$
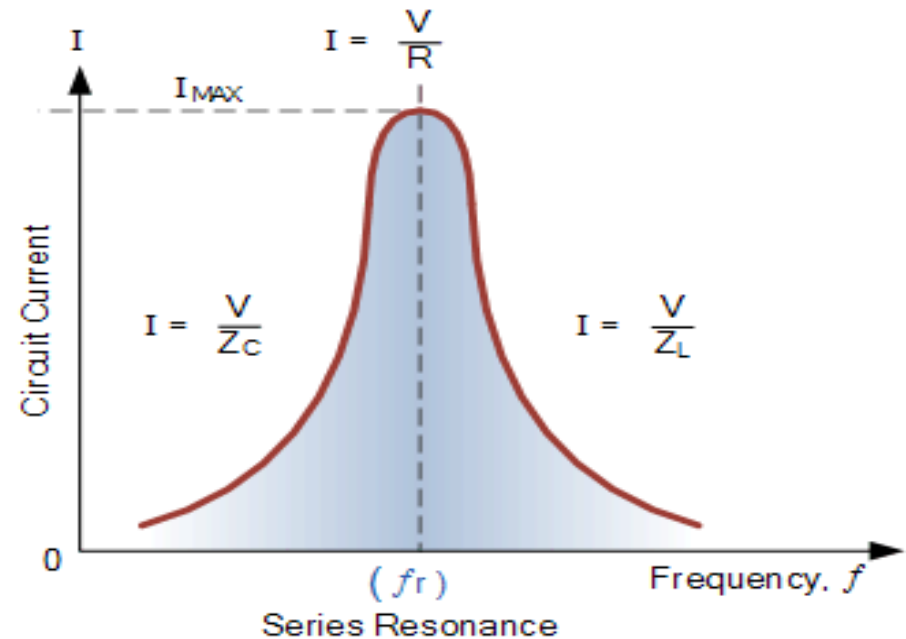
# Resonance Curve

- The curve obtained by plotting a graph between current and frequency is known as resonance curve or response curve .
- The current has a maximum value at resonance given by  $I_{\max} = V/R$ .
- The value of  $I$  decreases on either sides of the resonance



**THANK YOU**