


UNIT IV: INTERFACING OF 8051 MICROCONTROLLER:

**LCD,
STEPPER MOTOR, ADC
AND DAC**

WHAT IS LCD?

- An LCD (Liquid crystal display) display is specifically manufactured to be used with microcontrollers, which means that it cannot be activated by standard IC circuits.
- It is used for displaying different messages on a miniature liquid crystal display.
- It displays all the letters of alphabet, Greek letters, punctuation marks, mathematical symbols etc. In addition, it is possible to display symbols made up by the user.
- Other useful features include automatic message shift (left and right), cursor appearance, LED backlight etc.

LCD INTERFACING WITH 8051

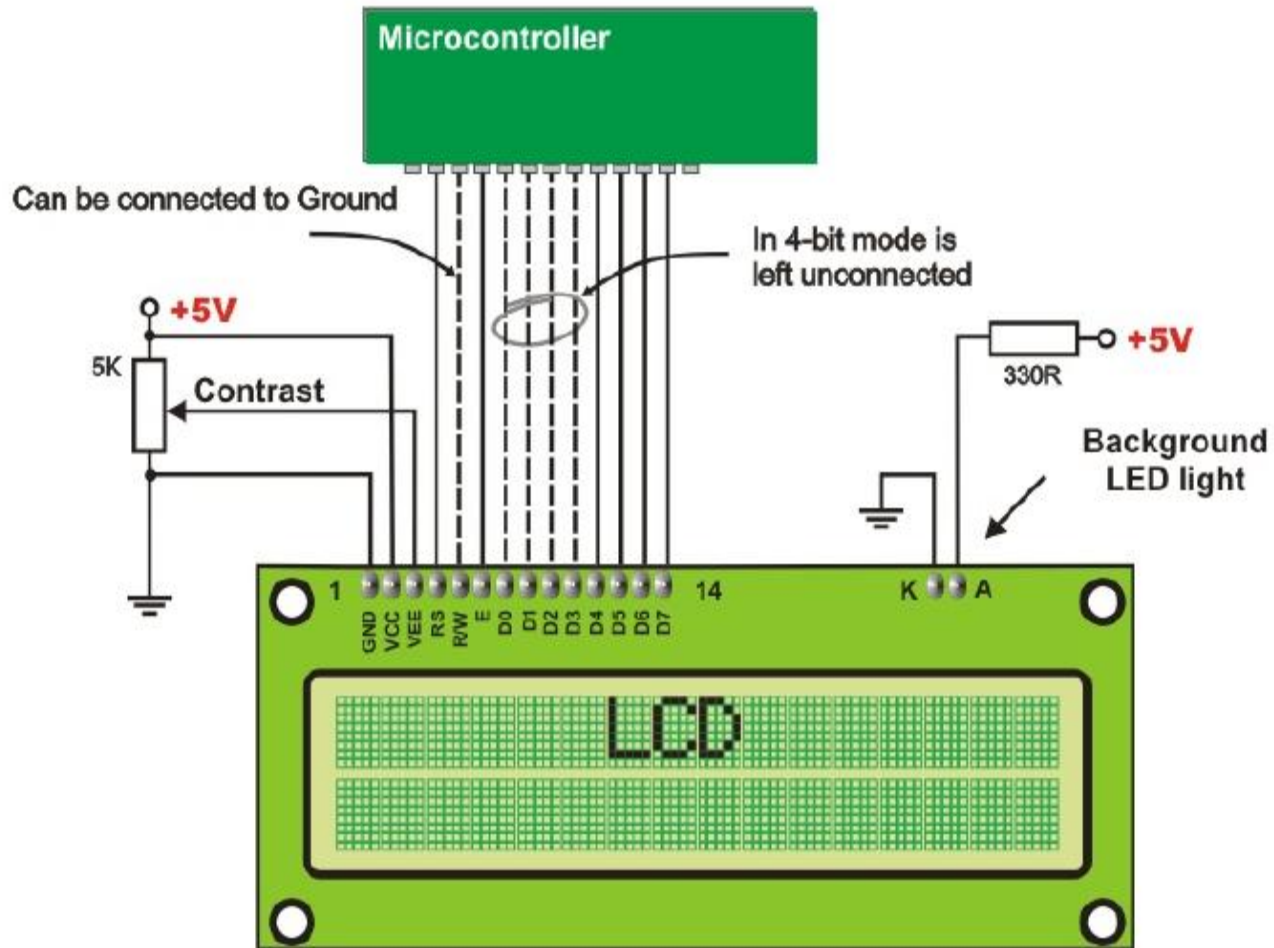

LCD PIN DESCRIPTION

Pin Descriptions for LCD

Pin	Symbol	I/O	Descriptions
1	VSS	--	Ground
2	VCC	--	+5V power supply
3	VEE	--	Power supply to control contrast
4	RS	I	RS=0 to select command register, RS=1 to select data register
5	R/W	I	R/W=0 for write, R/W=1 for read
6	E	I/O	Enable
7	DB0	I/O	The 8-bit data bus
8	DB1	I/O	The 8-bit data bus
9	DB2	I/O	The 8-bit data bus
10	DB3	I/O	The 8-bit data bus
11	DB4	I/O	The 8-bit data bus
12	DB5	I/O	The 8-bit data bus
13	DB6	I/O	The 8-bit data bus
14	DB7	I/O	The 8-bit data bus

- Send displayed information or instruction command codes to the LCD
- Read the contents of the LCD's internal registers

used by the LCD to latch information presented to its data bus

LCD COMMANDS

LCD Command Codes

Code (Hex)	Command to LCD Instruction Register
1	Clear display screen
2	Return home
4	Decrement cursor (shift cursor to left)
6	Increment cursor (shift cursor to right)
5	Shift display right
7	Shift display left
8	Display off, cursor off
A	Display off, cursor on
C	Display on, cursor off
E	Display on, cursor blinking
F	Display on, cursor blinking
10	Shift cursor position to left
14	Shift cursor position to right
18	Shift the entire display to the left
1C	Shift the entire display to the right
80	Force cursor to beginning to 1st line
C0	Force cursor to beginning to 2nd line
38	2 lines and 5x7 matrix

LCD INTERFACING C CODE

Example 12-2

Write an 8051 C program to send letters 'M', 'D', and 'E' to the LCD using the busy flag method.

Solution:

```
#include <reg51.h>
sfr ldata = 0x90; //P1=LCD data pins
sbit rs = P2^0;
sbit rw = P2^1;
sbit en = P2^2;
sbit busy = P1^7;
void main() {
    lcdcmd(0x38);
    lcdcmd(0x0E);
    lcdcmd(0x01);
    lcdcmd(0x06);
    lcdcmd(0x86);    //line 1, position 6
    lcdcmd('M');
    lcdcmd('D');
    lcdcmd('E');
}
.....
```

C CODE CONTD

```
void lcdcmd(unsigned char value){
    lcdready();          //check the LCD busy flag
    ldata = value;       //put the value on the pins
    rs = 0;
    rw = 0;
    en = 1;              //strobe the enable pin
    MSDelay(1);
    en = 0;
    return;
}

void lcddata(unsigned char value){
    lcdready();          //check the LCD busy flag
    ldata = value;       //put the value on the pins
    rs = 1;
    rw = 0;
    en = 1;              //strobe the enable pin
    MSDelay(1);
    en = 0;
    return;
}
.....
```

C CODECONTD

```
void lcdready() {  
    busy = 1;           //make the busy pin at input  
    rs = 0;  
    rw = 1;  
    while(busy==1) {    //wait here for busy flag  
        en = 0;         //strobe the enable pin  
        MSDelay(1);  
        en = 1;  
    }  
  
void lcddata(unsigned int itime) {  
    unsigned int i, j;  
    for(i=0; i<itime; i++)  
        for(j=0; j<1275; j++);  
}
```


LCD ASSEMBLY CODE

To send any of the commands to the LCD, make pin RS=0. For data, make RS=1. Then send a high-to-low pulse to the E pin to enable the internal latch of the LCD. This is shown in the code below.

```
;calls a time delay before sending next data/command
;P1.0-P1.7 are connected to LCD data pins D0-D7
;P2.0 is connected to RS pin of LCD
;P2.1 is connected to R/W pin of LCD
;P2.2 is connected to E pin of LCD
```

```
ORG      0H
MOV      A,#38H    ;INIT. LCD 2 LINES, 5X7 MATRIX
ACALL    COMNWRT   ;call command subroutine
ACALL    DELAY     ;give LCD some time
MOV      A,#0EH    ;display on, cursor on
ACALL    COMNWRT   ;call command subroutine
ACALL    DELAY     ;give LCD some time
MOV      A,#01     ;clear LCD
ACALL    COMNWRT   ;call command subroutine
ACALL    DELAY     ;give LCD some time
MOV      A,#06H    ;shift cursor right
ACALL    COMNWRT   ;call command subroutine
ACALL    DELAY     ;give LCD some time
MOV      A,#84H    ;cursor at line 1, pos. 4
ACALL    COMNWRT   ;call command subroutine
ACALL    DELAY     ;give LCD some time
```

```

        MOV     A,#'N'      ;display letter N
        ACALL  DATAWRT    ;call display subroutine
        ACALL  DELAY       ;give LCD some time
        MOV     A,#'O'      ;display letter O
        ACALL  DATAWRT    ;call display subroutine
AGAIN:   SJMP   AGAIN      ;stay here
COMNWRT:                ;send command to LCD
        MOV     P1,A        ;copy reg A to port 1
        CLR     P2.0        ;RS=0 for command
        CLR     P2.1        ;R/W=0 for write
        SETB    P2.2        ;E=1 for high pulse
        ACALL  DELAY       ;give LCD some time
        CLR     P2.2        ;E=0 for H-to-L pulse
        RET

DATAWRT:                ;write data to LCD
        MOV     P1,A        ;copy reg A to port 1
        SETB    P2.0        ;RS=1 for data
        CLR     P2.1        ;R/W=0 for write
        SETB    P2.2        ;E=1 for high pulse
        ACALL  DELAY       ;give LCD some time
        CLR     P2.2        ;E=0 for H-to-L pulse
        RET

DELAY:   MOV     R3,#50      ;50 or higher for fast CPUs
HERE2:   MOV     R4,#255     ;R4 = 255
HERE:    DJNZ    R4,HERE     ;stay until R4 becomes 0
        DJNZ    R3,HERE2
        RET
        END

```

ASSEMBLY CODE contd

```
;Check busy flag before sending data, command to LCD
;P1=data pin
;P2.0 connected to RS pin
;P2.1 connected to R/W pin
;P2.2 connected to E pin
    ORG      0H
    MOV      A,#38H           ;init. LCD 2 lines ,5x7 matrix
    ACALL    COMMAND          ;issue command
    MOV      A,#0EH           ;LCD on, cursor on
    ACALL    COMMAND          ;issue command
    MOV      A,#01H           ;clear LCD command
    ACALL    COMMAND          ;issue command
    MOV      A,#06H           ;shift cursor right
    ACALL    COMMAND          ;issue command
    MOV      A,#86H           ;cursor: line 1, pos. 6
    ACALL    COMMAND          ;command subroutine
    MOV      A,#'N'           ;display letter N
    ACALL    DATA_DISPLAY
    MOV      A,#'O'           ;display letter O
    ACALL    DATA_DISPLAY
HERE: SJMP    HERE            ;STAY HERE
```


COMMAND:

```
ACALL READY      ;is LCD ready?
MOV P1,A         ;issue command code
CLR P2.0         ;RS=0 for command
CLR P2.1         ;R/W=0 to write to LCD
SETB P2.2        ;E=1 for H-to-L pulse
CLR P2.2         ;E=0, latch in
RET
```

DATA_DISPLAY:

```
ACALL READY      ;is LCD ready?
MOV P1,A         ;issue data
SETB P2.0        ;RS=1 for data
CLR P2.1         ;R/W=0 to write to LCD
SETB P2.2        ;E=1 for H-to-L pulse
CLR P2.2         ;E=0, latch in
RET
```

READY:

```
SETB P1.7        ;make P1.7 input port
CLR P2.0         ;RS=0 access command reg
SETB P2.1        ;R/W=1 read command reg
;read command reg and check busy flag
BACK:SETB P2.2    ;E=1 for H-to-L pulse
CLR P2.2         ;E=0 H-to-L pulse
JB P1.7,BACK     ;stay until busy flag=0
```


```
RET
END
```

To read the command register, we make R/W=1, RS=0, and a H-to-L pulse for the E pin.

If bit 7 (busy flag) is high, the LCD is busy and no information should be issued to it.

LCD READ OPERATION

LCD Timing for Read

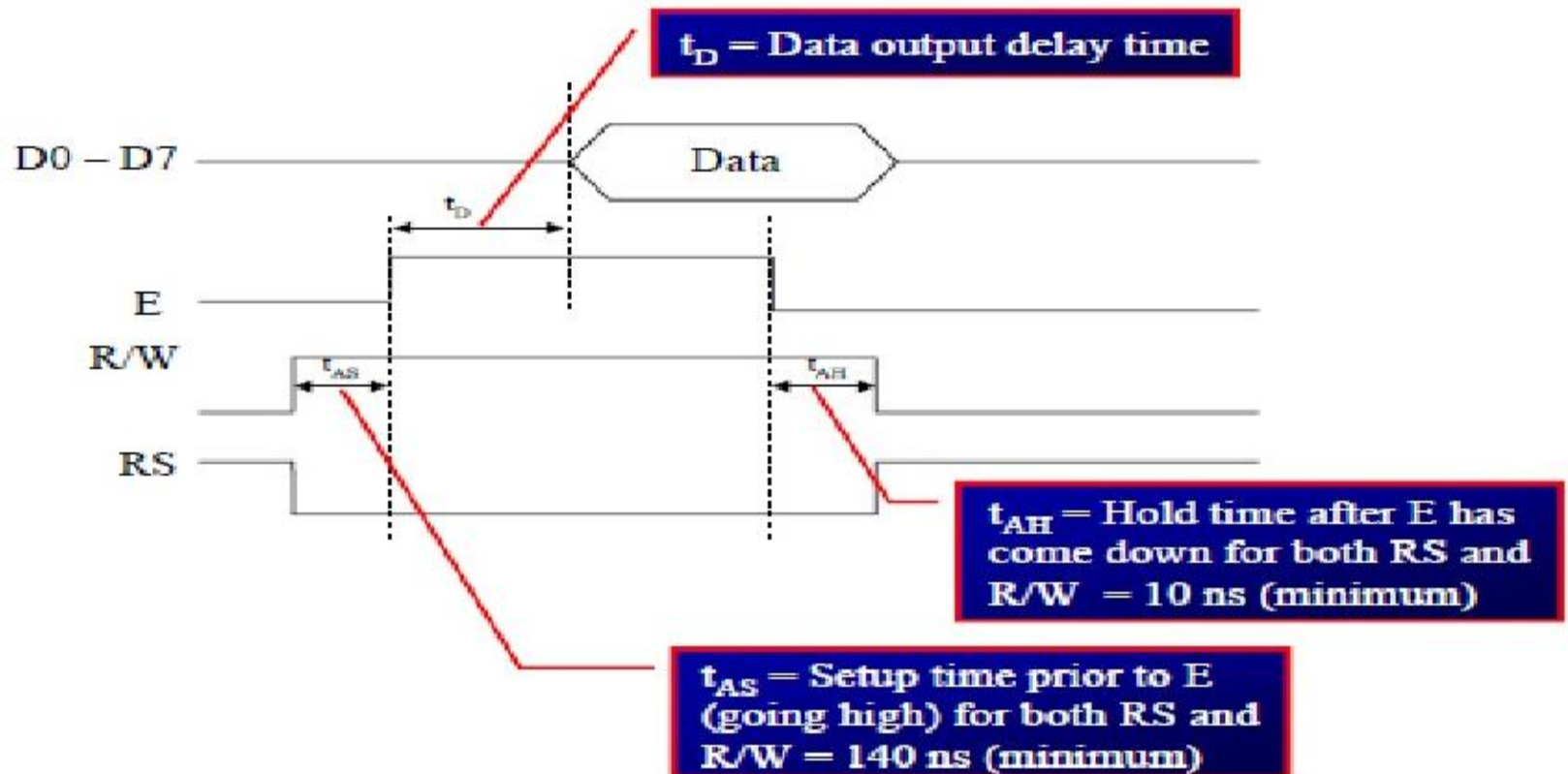


Note : Read requires an L-to-H pulse for the E pin

LCD WRITE OPERATION

LCD Timing for Write

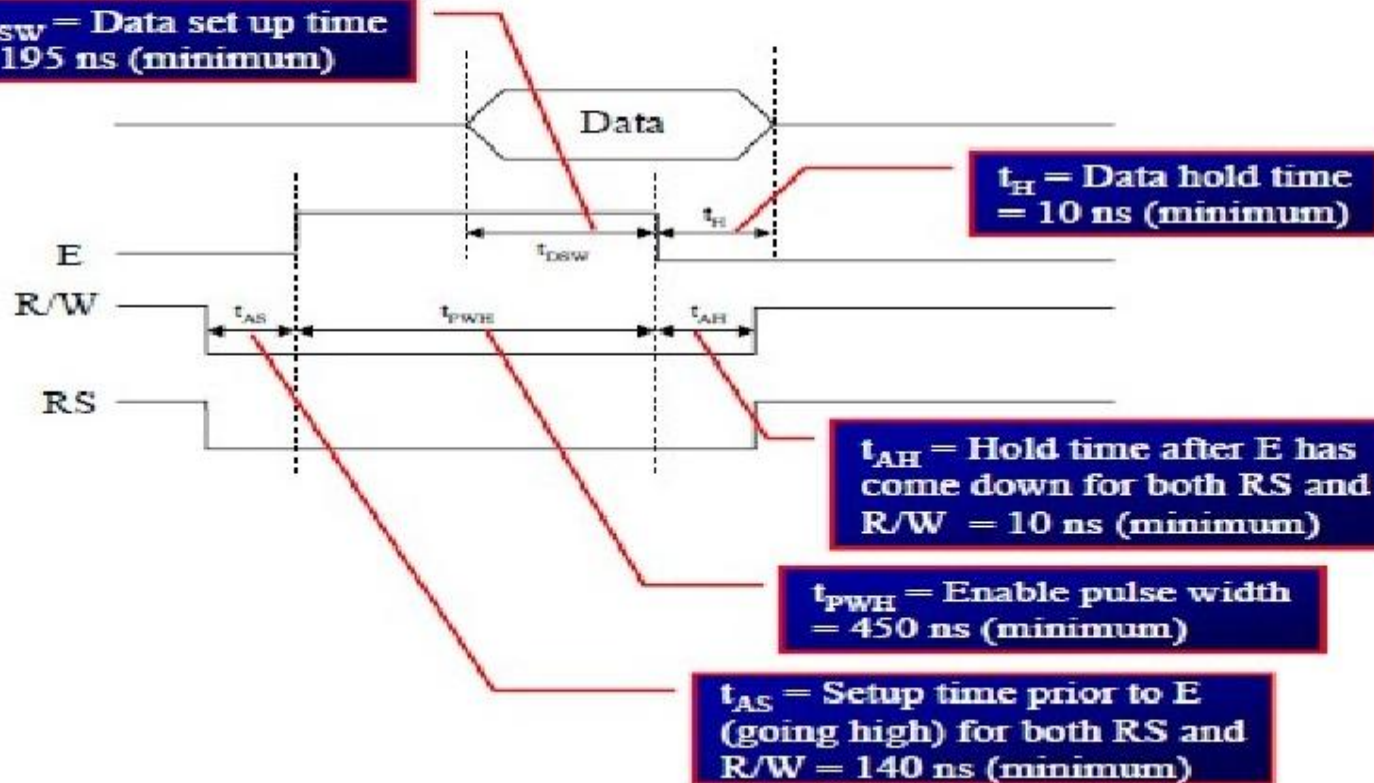t_{DSW} = Data set up time
= 195 ns (minimum)




STEPPER MOTOR

- A *stepper motor* is an electromechanical device which converts electrical pulses into discrete mechanical movements or steps.
- This motor divides a full rotation of 360 degrees into a number of equal steps.

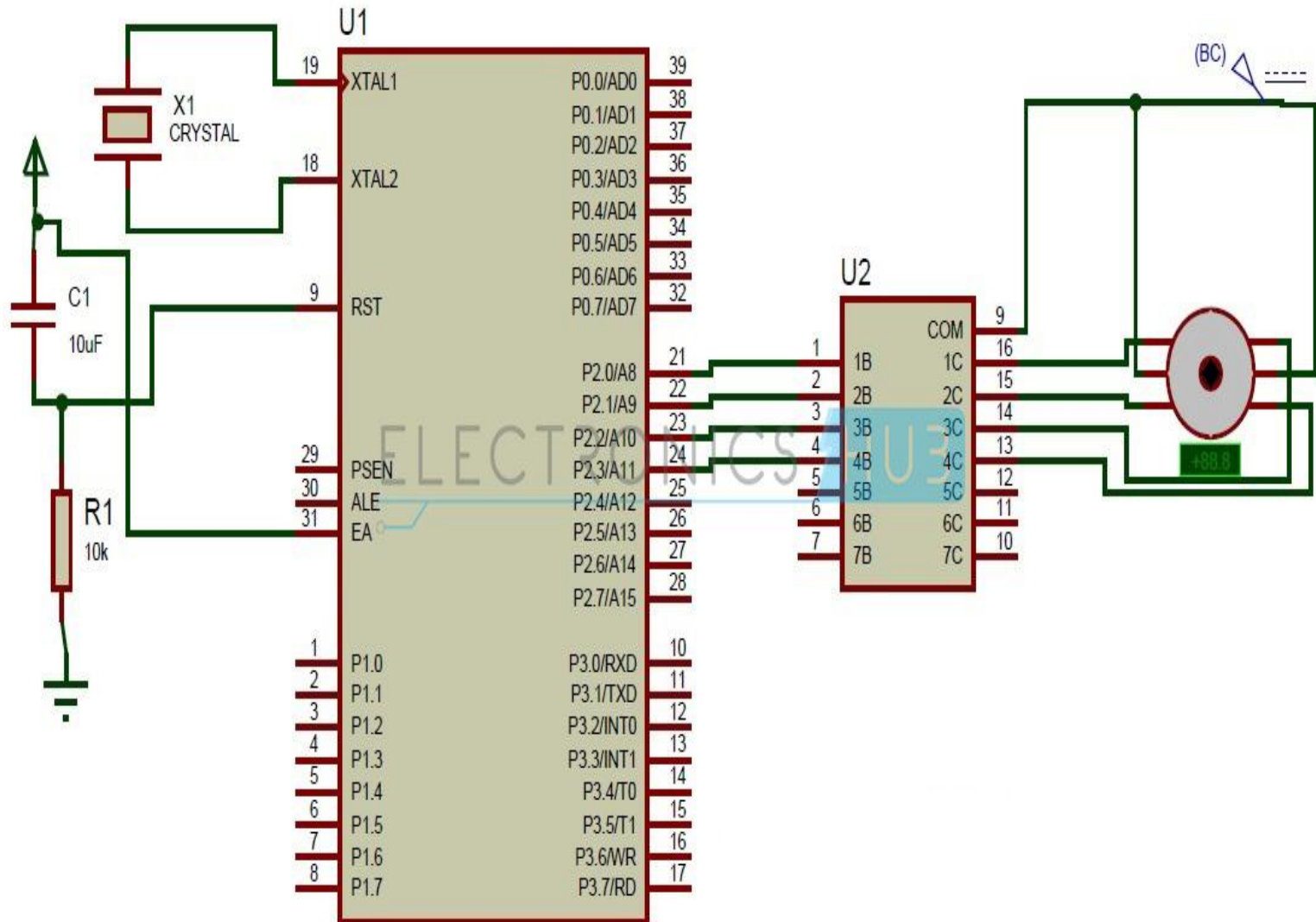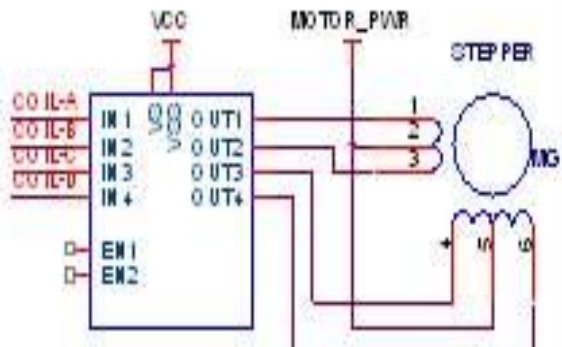

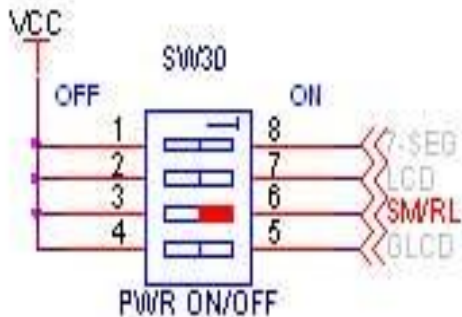
INTERFACING STEPPER MOTOR WITH 8051

- We now want to control a stepper motor in 8051 . It works by turning ON & OFF a four I/O port lines generating at a particular frequency.
- The 8051 has four numbers of I/O port lines, connected with I/O Port lines (P0.0 – P0.3) to rotate the stepper motor.
- ULN2003 is a high voltage and high current Darlington array IC.
- ULN2003 is used as a driver for port I/O lines, drivers output connected to stepper motor, connector provided for external power supply if needed.

INTERFACING DIAGRAM



Pin Assignment with 8051

	Stepper Motor(5V)	8051 Lines	Stepper Motor PWR Select
STEPPER MOTOR	COIL-A	P0.0	 <p>JP3</p> <p>1 2 3 Internal +5V (Driver section)</p>
	COIL-B	P0.1	
	COIL-C	P0.2	
	COIL-D	P0.3	
 <p>Make switch SW30 to <i>SM/RL</i> label marking position.</p>			 <p>SW30</p> <p>PWR ON/OFF</p>


Full step and half step sequence

- **In the full step sequence**, two coils are energized at the same time and motor shaft rotates. The order in which coils has to be energized is given in the table below.
- **In Half mode step sequence**, motor step angle reduces to half the angle in full mode. So the angular resolution is also increased i.e. it becomes double the angular resolution in full mode. Also in half mode sequence the number of steps gets doubled as that of full mode. Half mode is usually preferred over full mode. Table below shows the pattern of energizing the coils.

Full step sequence

Full Mode Sequence				
Step	A	B	A\	B\
0	1	1	0	0
1	0	1	1	0
2	0	0	1	1
3	1	0	0	1

Full step sequence

 

Lead Unipolar Driver

Unipolar control is the most simple and cost-effective way to drive a stepper motor, but results in approximately 30% less torque in comparison to the nowadays widely used bipolar drivers. Since the cost advantage is very small today due to cheap integrated circuits, bipolar drivers are now used in most new applications.


Stepmode

F	0	1	2	3				
H	0	1	2	3	4	5	6	7
A	1	0	0	0	0	0	1	1
B	1	1	1	0	0	0	0	0
A'	0	0	1	1	1	0	0	0
B'	0	0	0	0	1	1	1	0
dez	12	4	6	2	3	1	9	8

Half step sequence

Half Mode Sequence				
Step	A	B	A\	B\
0	1	1	0	0
1	0	1	0	0
2	0	1	1	0
3	0	0	1	0
4	0	0	1	1
5	0	0	0	1
6	1	0	0	1
7	1	0	0	0

Half step sequence

 

Lead Unipolar Driver

Unipolar control is the most simple and cost-effective way to drive a stepper motor, but results in approximately 30% less torque in comparison to the nowadays widely used bipolar drivers. Since the cost advantage is very small today due to cheap integrated circuits, bipolar drivers are now used in most new applications.

Stepmode

F	0	1	2	3				
H	0	1	2	3	4	5	6	7
A	1	0	0	0	0	0	1	1
B	1	1	1	0	0	0	0	0
A'	0	0	1	1	1	0	0	0
B'	0	0	0	0	1	1	1	0
dez	12	4	6	2	3	1	9	8

C Program to control stepper motor using 8051

- ```
#include <reg51.h> //Define 8051 registers
#include<stdio.h>
void DelayMs(unsigned int); //Delay function\

//-----

// Main Program

//-----
void Clockwise (void)
{
 unsigned int i;
 for (i=0;i<30;i++)
 {
 P0 = 0x01;DelayMs(5); //Delay 20msec
 P0 = 0x02;DelayMs(5);
 P0 = 0x04;DelayMs(5);
 P0 = 0x08;DelayMs(5);
 }
}
```

# C Program to Control Stepper Motor using 8051 Contd....

- ```
void AntiClockwise (void)
{
    unsigned int i;
    for (i=0;i<30;i++)
    {
        P0 = 0x08;DelayMs(5);      //Delay 20msec
        P0 = 0x04;DelayMs(5);
        P0 = 0x02;DelayMs(5);
        P0 = 0x01;DelayMs(5);
    }
}

void main (void)
{
    P0 = 0;                        //Initialize Port0

    while(1)                       //Loop Forever
    {
        Clockwise ();
        DelayMs (100);
        P0 = 0;
        AntiClockwise ();
        DelayMs (100);
        P0 = 0;
    }
}
```

STEPPER MOTOR ASSEMBLY CODE

org 0H

stepper **equ** P1

main:

mov stepper, #0CH

acall delay

mov stepper, #06H

acall delay

mov stepper, #03H

acall delay

mov stepper, #09H

acall delay

sjmp main

ASSEMBLY CODE CONTD

delay:

mov r7,#4

wait2:

mov r6,#0FFH

wait1:

mov r5,#0FFH

wait:

djnz r5,wait

djnz r6,wait1

djnz r7,wait2


ret

end


Interfacing ADC to 8051

- 8051 microcontroller it doesn't have an On chip ADC to accept the digital input, it will not accept analog input.
- so we need a ADC to process the analog signal.
- For interfacing ADC 0809 we require 8 data lines.
- So ADC 0809 is an 8 bit ADC has 8 channels works on successive approximation conversion technique.

PIN ASSIGNMENT WITH 8051

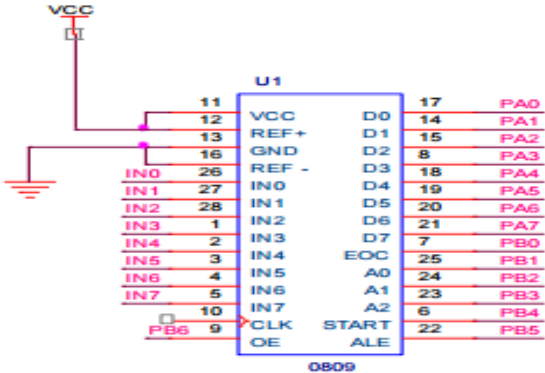	20PIN CONNECTOR	ADC 0809	ADC 0809
Data lines	PA.0	D0	 <p>PA0 – PA7 is connected to 8 no's of LED</p>
	PA.1	D1	
	PA.2	D2	
	PA.3	D3	
	PA.4	D4	
	PA.5	D5	
	PA.6	D6	
	PA.7	D7	
Control Lines	PB.0	EOC	
	PB.1	A0	
	PB.2	A1	
	PB.3	A2	
	PB.4	Start	
	PB.5	ALE	
	PB.6	OE	
	PB.7	NC	
PWR	17,19	Vcc	Supply form 8051/8086/80805 trainer Kit
	18,20	Gnd	

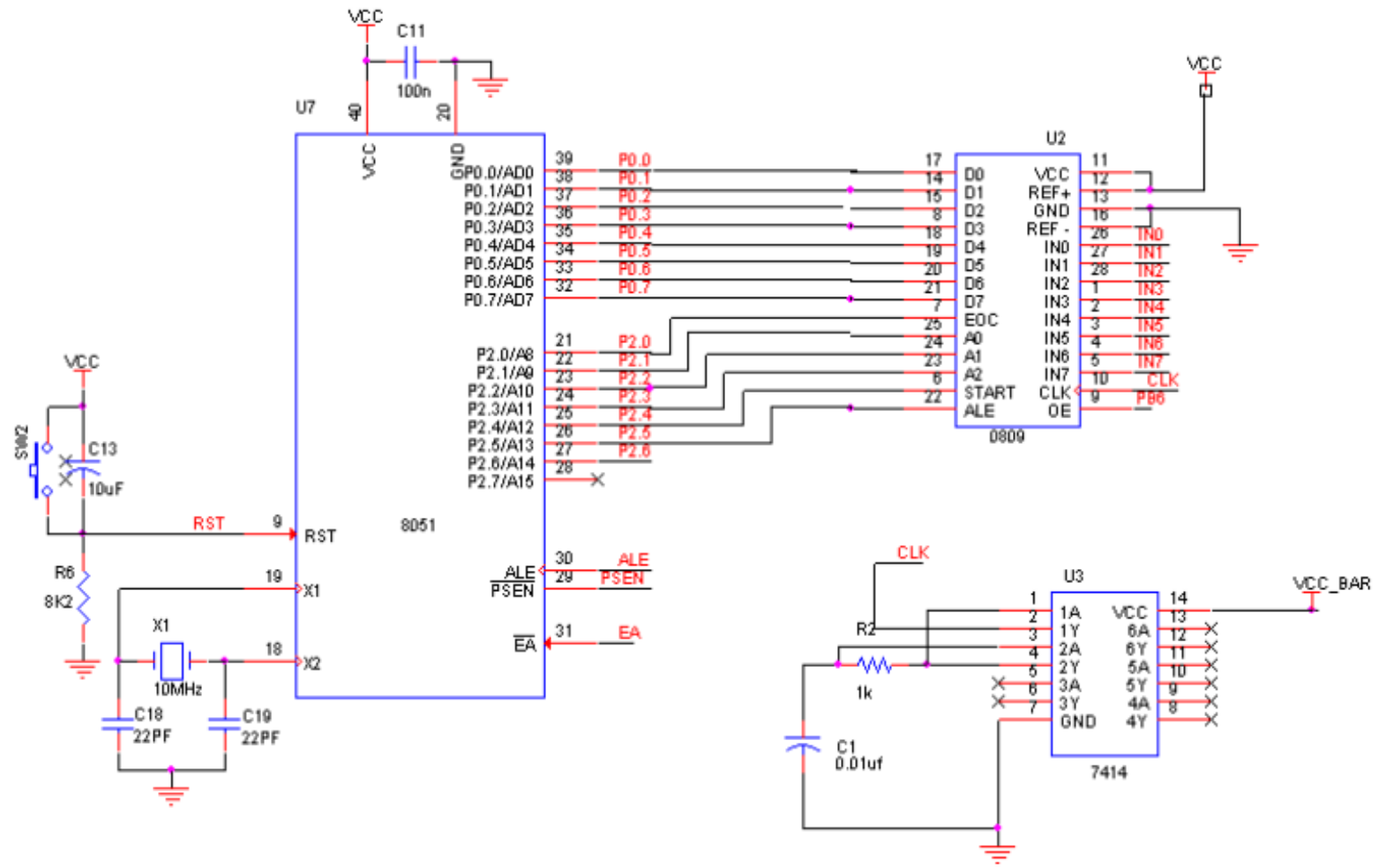CIRCUIT DIAGRAM TO INTERFACE ADC 0809 WITH 8051



8051 Assembly Code

```
ale equ P3.4
oe equ P3.7
start equ P3.5
eoc equ P3.6
sel_a equ P3.1
sel_b equ P3.2
sel_c equ P3.3
adc_data equ P1
org 0H
;Data port to input
mov adc_data, #0FFH
;EOC as Input
setb eoc
;rest of output signals
clr ale
clr oe
clr start
main_loop:
;Select Analog Channel 1
setb sel_a
clr sel_b
clr sel_c
;Latch channel select
setb ale
```

8051 Assembly Code Contd...

;Start conversion

setb start

clr ale

clr start

;Wait for end of conversion

jb eoc, \$; \$ means jump to same location

jnb eoc, \$

;Assert read signal

setb oe

; Read Data

mov A, adc_data

clr oe

;ADC data is now in accumulator

;Start over for next conversion

sjmp main_loop


end

DAC Interfacing with 8051

- Microcontroller are used in wide variety of applications like for measuring and control of physical quantity like temperature, pressure, speed, distance, etc.
- In these systems microcontroller generates output which is in digital form but the controlling system requires analog signal as they don't accept digital data thus making it necessary to use DAC which converts digital data into equivalent analog voltage.
- The IC DAC0808 converts digital data into equivalent analog Current. Hence we require an I to V converter to convert this current into equivalent voltage.
- According to theory of DAC Equivalent analog output is given as:

$$V_0 = V_{ref} \left[\frac{D_0}{2} + \frac{D_1}{4} + \frac{D_2}{8} + \frac{D_3}{16} + \frac{D_4}{32} + \frac{D_5}{64} + \frac{D_6}{128} + \frac{D_7}{256} \right]$$

Interfacing Diagram

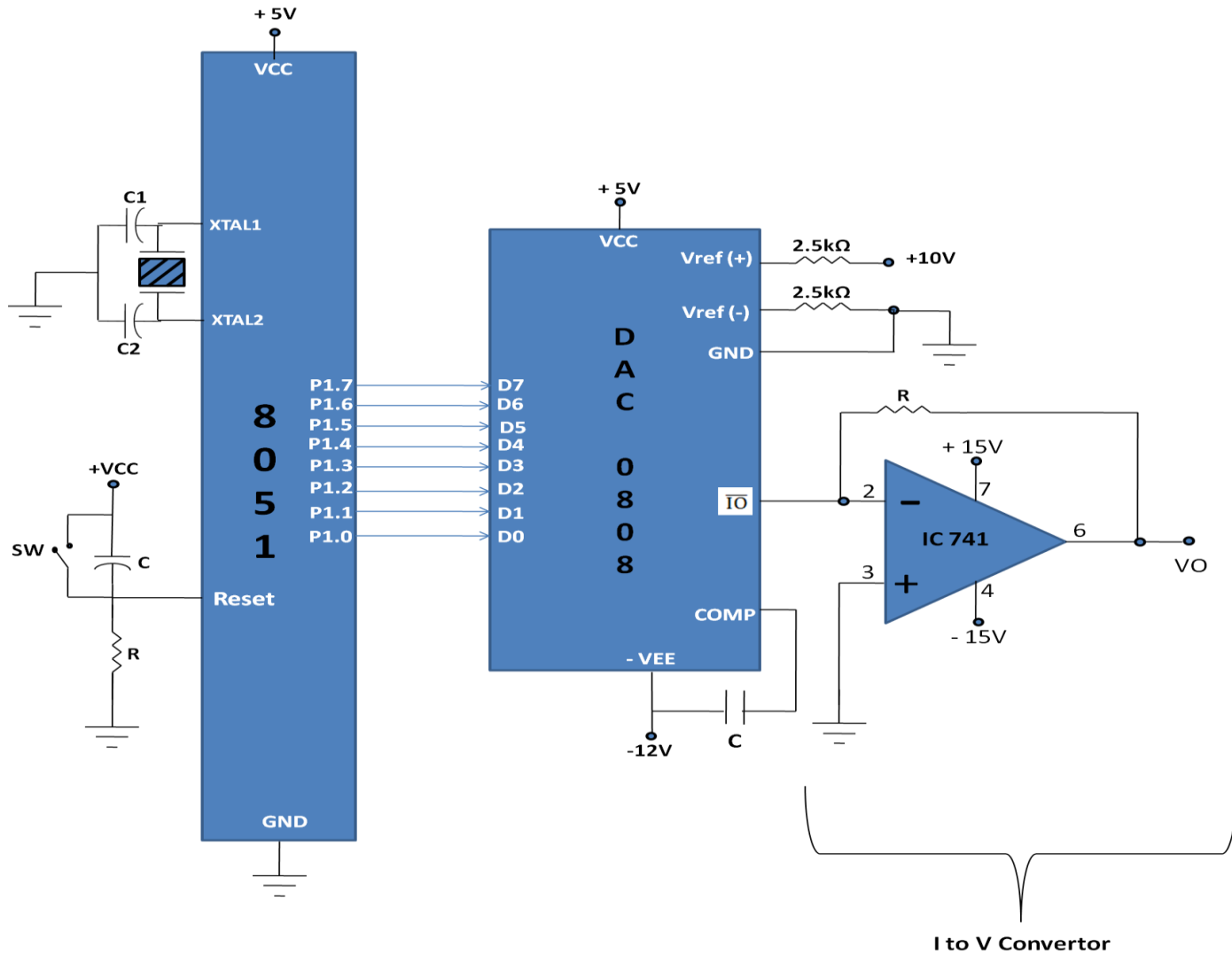

To generate triangular waveform using DAC.

Program

```

                                MOV  DPTR, #FFC8
START                          MOV  A, #00
LOOP1                          MOV  @DPTR,A
                                INC   A
                                JNZ   LOOP1
                                MOV  A, #FF
LOOP2                          MOVX @DPTR,A
                                DEC   A
                                JNZ   LOOP2
                                LJMP  START
```

To generate square wave using DAC.

PROGRAM

```
START      MOV  DPTR,#FFC8
            MOV  A,#00
            MOVX @DPTR,A
            LCALL DELAY
            MOV  A,#FF
            MOVX @DPTR,A
            LCALL DELAY
            LJMP START
DELAY      MOV  R1, #05
LOOP      MOV  R2, #FF
HERE      DJNZ  R2, HERE
            DJNZ  R1, LOOP
            RET
```