 


# Logic Gates

## LOGIC OPERATIONS & GATES

The basic operations are AND, OR, NOT, and FLIP-FLOP.

# AND



$$\begin{aligned} Y &= A \text{ AND } B \text{ AND } C \dots \text{ AND } N \\ &= A \cdot B \cdot C \cdot \dots \cdot N \\ &= ABC \dots N \end{aligned} \quad (1.1)$$

Fig. 1.2     *The Standard Symbol*  
- - - - -     *for an AND Gate*

where  $A, B, C, \dots, N$  are the input variables and  $Y$  is the output variable.

Equation (1.1) is known as the *Boolean equation* or the *logical equation* of the AND gate.

# OR

 


Fig. 1.5    *The Standard Symbol for  
an OR Gate*

$$Y = A \text{ OR } B \text{ OR } C \dots \text{ OR } N = A + B + C + \dots + N \quad (1.2)$$

Table 1.2    *Truth Table of a 2-Input OR Gate*

Inputs		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	1

# NOT

 


Fig. 1.7 The Standard Symbols for a NOT Gate

$$Y = \text{NOT } A$$

$$= \overline{A}$$

“Y equals NOT A” or “Y equals complement of A”. The NOT operation is also referred to as an *inversion* or *complementation*. The presence of a small circle, known as the *bubble*, always denotes inversion in digital circuits.

Table 1.3 Truth Table of a NOT Gate

Input	Output
A	Y
0	1
1	0

# NAND AND NOR OPERATIONS

## NAND

The NOT–AND operation is known as the NAND operation.

$$Y' = AB \dots N \qquad Y = \overline{Y'} = \overline{AB \dots N}$$


 


Fig. 1.10 (a) **NAND Operation as NOT–AND Operation,**  
 ----- (b) **Standard Symbol for the NAND Gate**



Table 1.4 Truth Table of a 2-Input **NAND** Gate

Inputs		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

 The three basic logic operations, AND, OR, and NOT can be performed by using only NAND gates. These are given in Fig. 1.11.



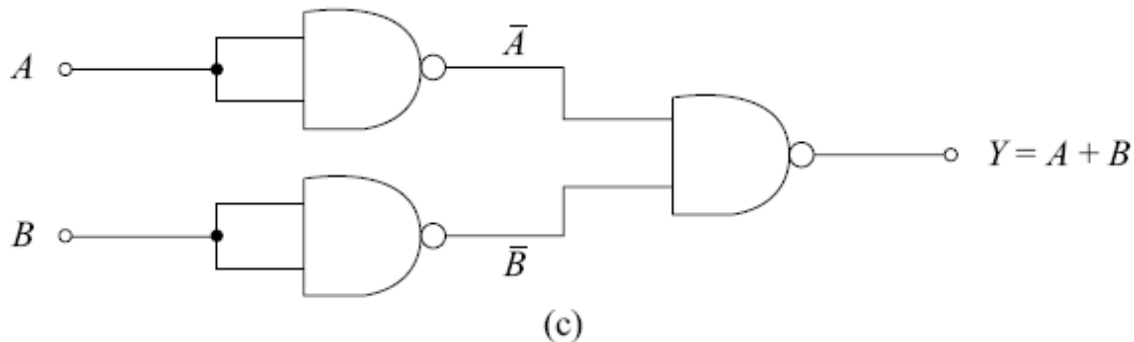 (a) Fig. 1.11 Realisation of Basic Logic Operations Using **NAND** Gates  
(a) NOT (b) AND (c) OR



### Example 1.6

If the voltage waveforms of Fig. 1.3 are applied at the inputs of a 2-input NAND gate, find the output waveform.

#### *Solution*

The output waveform will be inverse of the output waveform  $Y$  of Fig. 1.4.

# NOR

The NOT–OR operation is known as the NOR operation.


 
 
 


Fig. 1.13 (a) **NOR Operation as NOT–OR Operation**  
 (b) **Standard Symbol for the NOR Gate**

Table 1.5 *Truth Table of a 2-Input NOR Gate*

Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 The three basic logic operations, AND, OR, and NOT can be performed by using only the NOR gates. These are given in Fig. 1.14.



### Example 1.8

If the voltage waveforms of Fig. 1.3 are applied at the inputs of a 2-input NOR gate, determine the output waveform.

#### *Solution*

The output waveform will be inverse of the output waveform of Fig. 1.6.



# EXCLUSIVE-OR

 


Fig. 1.15    *Standard Symbol for EX-OR Gate*

$$Y = A \text{ EX-OR } B = A \oplus B$$

Table 1.6    *Truth Table of EX-OR Gate*

Inputs		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

# EXCLUSIVE-NOR

 


Fig. 1.17 *Standard Symbol for EX-NOR Gate*

$$Y = A \text{ EX-NOR } B = \overline{A \text{ EX-OR } B} = \overline{A \oplus B} = A \odot B$$

Table 1.7 *Truth Table of EX-NOR Gate*

Inputs		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

# *Boolean Algebraic Theorems*

Theorem No.	Theorem
1.1	$A + 0 = A$
1.2	$A \cdot 1 = A$
1.3	$A + 1 = 1$
1.4	$A \cdot 0 = 0$
1.5	$A + A = A$
1.6	$A \cdot A = A$
1.7	$A + \bar{A} = 1$
1.8	$A \cdot \bar{A} = 0$
1.9	$A \cdot (B + C) = AB + AC$
1.10	$A + BC = (A + B)(A + C)$
1.11	$A + AB = A$

(Continued)

Theorem No.	Theorem
1.12	$A(A + B) = A$
1.13	$A + \overline{A}B = (A + B)$
1.14	$A(\overline{A} + B) = AB$
1.15	$AB + A\overline{B} = A$
1.16	$(A + B) \cdot (A + \overline{B}) = A$
1.17	$AB + \overline{A}C = (A + C)(\overline{A} + B)$
1.18	$(A + B)(\overline{A} + C) = AC + \overline{A}B$
1.19	$AB + \overline{A}C + BC = AB + \overline{A}C$
1.20	$(A + B)(\overline{A} + C)(B + C) = (A + B)(\overline{A} + C)$
1.21	$\overline{A \cdot B \cdot C \cdot \dots} = \overline{A} + \overline{B} + \overline{C} + \dots$
1.22	$\overline{A + B + C + \dots} = \overline{A} \cdot \overline{B} \cdot \overline{C} \dots$

# **Combinational Logic Design**

## **Basically, Digital circuits are divided into two broad categories**

1. Combinational circuits, and
2. Sequential circuits

In combinational circuits, the output at any instant of time depend upon the inputs present at that instant of time. This means there is no memory in these circuits. There are other types of circuits in which the outputs at any instant of time depend upon the present inputs as well as past inputs/outputs. This means that there are elements used to store past information. These elements are known as memory. Such circuits are known as sequential circuits.

The design requirements of combinational circuits may be specified in one of the following ways:

1. A set of statements,
2. Boolean expression, and
3. Truth table

The following methods can be used to simplify the boolean functions:

1. Algebraic method
2. Karnaugh-map technique,
3. Quine-McCluskey method, and
4. Variable entered mapping (VEM) technique

# KARNAUGH MAP REPRESENTATION OF LOGIC FUNCTIONS

$B \backslash A$	0	1
0	0	2
1	1	3

(a)

$C \backslash AB$	00	01	11	10
0	0	2	6	4
1	1	3	7	5

(b)

$CD \backslash AB$	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

(c)

Fig. 5.5 Karnaugh-maps (a) Two-variable  
 ----- (b) Three-variable (c) Four-variable

$A$		0	1
$B$	0	$\bar{A}\bar{B}$	$A\bar{B}$
	1	$\bar{A}B$	$AB$

(a)

$A$		0	1
$B$	0	$A + B$	$\bar{A} + B$
	1	$A + \bar{B}$	$\bar{A} + \bar{B}$

(b)

$AB$		00	01	11	10
$C$	0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
	1	$\bar{A}\bar{B}C$	$\bar{A}BC$	$ABC$	$A\bar{B}C$

(c)

$AB$		00	01	11	10
$C$	0	$A + B + C$	$A + \bar{B} + C$	$\bar{A} + \bar{B} + C$	$\bar{A} + B + C$
	1	$A + B + \bar{C}$	$A + \bar{B} + \bar{C}$	$\bar{A} + \bar{B} + \bar{C}$	$\bar{A} + B + \bar{C}$

(d)



$AB \backslash CD$		00	01	11	10
$CD$	00	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}B\bar{C}\bar{D}$	$AB\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$
	01	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}B\bar{C}D$	$AB\bar{C}D$	$A\bar{B}\bar{C}D$
	11	$\bar{A}\bar{B}CD$	$\bar{A}BCD$	$ABCD$	$A\bar{B}CD$
	10	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$ABC\bar{D}$	$A\bar{B}C\bar{D}$

(e)

$AB \backslash CD$		00	01	11	10
$CD$	00	$A + B + C + D$	$A + \bar{B} + C + D$	$\bar{A} + \bar{B} + C + D$	$\bar{A} + B + C + D$
	01	$A + B + C + \bar{D}$	$A + \bar{B} + C + \bar{D}$	$\bar{A} + \bar{B} + C + \bar{D}$	$\bar{A} + B + C + \bar{D}$
	11	$A + B + \bar{C} + \bar{D}$	$A + \bar{B} + \bar{C} + \bar{D}$	$\bar{A} + \bar{B} + \bar{C} + \bar{D}$	$\bar{A} + B + \bar{C} + \bar{D}$
	10	$A + B + \bar{C} + D$	$A + \bar{B} + \bar{C} + D$	$\bar{A} + \bar{B} + \bar{C} + D$	$\bar{A} + B + \bar{C} + D$

(f)

Maxterm/Minterm Corresponding to Each Cell of K-maps

## Design Examples

### Arithmetic Circuits

Truth Table of Half-adder

Inputs		Outputs	
$A$	$B$	$S$	$C$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the truth table, we obtain the logical expressions for  $S$  and  $C$  outputs as  
 $S = \bar{A}B + A\bar{B} = A \oplus B$ ,  $C = AB$

 


Fig. 5.19

*Realisation of an Half-adder*


## Full-adder

$$S_n = \bar{A}_n B_n \bar{C}_{n-1} + \bar{A}_n \bar{B}_n C_{n-1} + A_n \bar{B}_n \bar{C}_{n-1} + A_n B_n C_{n-1}$$


$$C_n = A_n B_n + B_n C_{n-1} + A_n C_{n-1}$$

***Truth Table of a Full-adder***

Inputs			Outputs	
$A_n$	$B_n$	$C_{n-1}$	$S_n$	$C_n$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

(a)

 

(b)

Fig. 5.20

-----

*K-maps for (a)  $S_n$  (b)  $C_n$*

## BCD-to-7-Segment Decoder

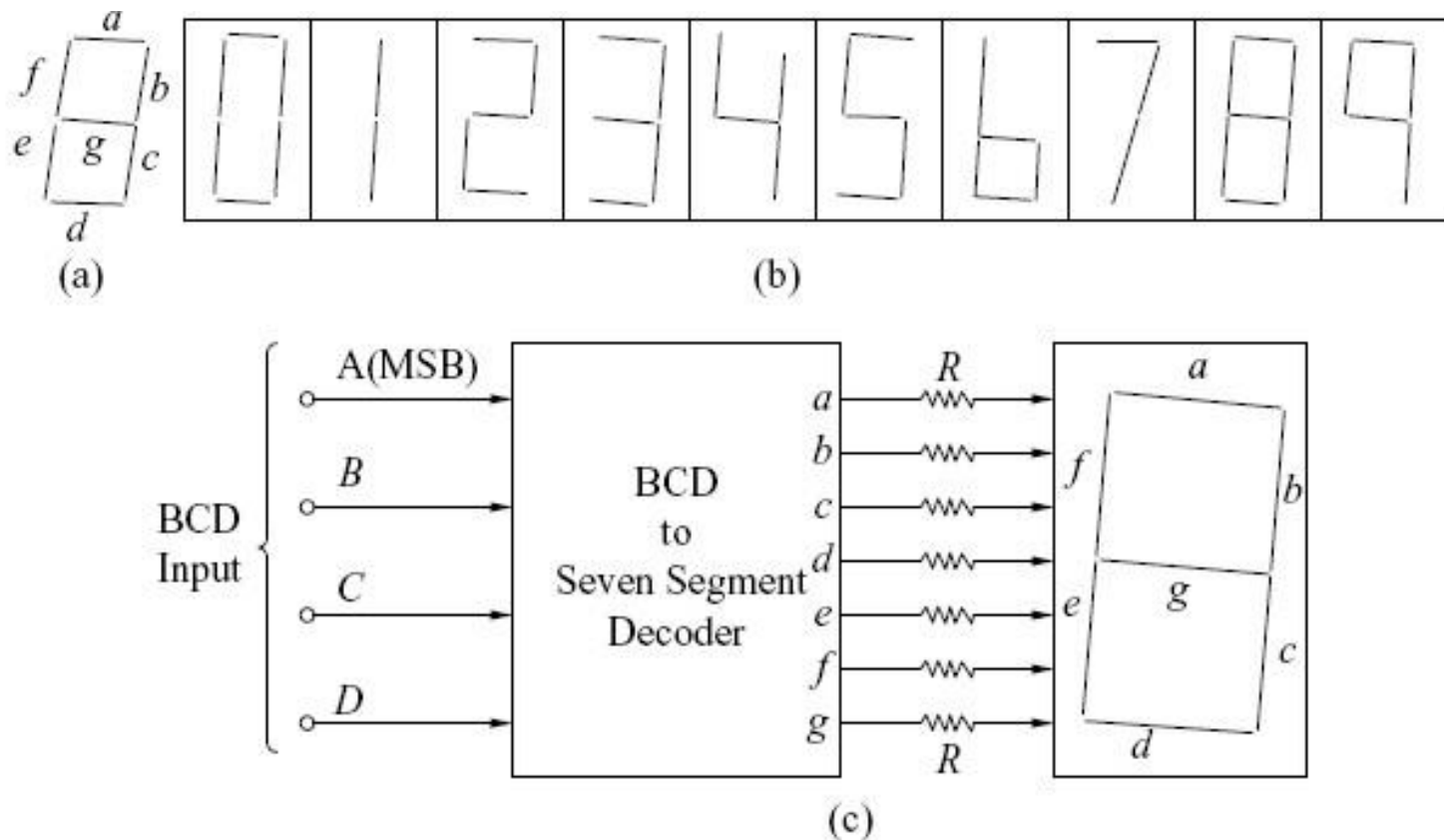


Fig. 5.24 (a) 7-segment Display (b) Display of Numerals (c) Display System

Truth Table of BCD-to-7 Segment Decoder

Decimal digit displayed	Inputs				Outputs						
	<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	0	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

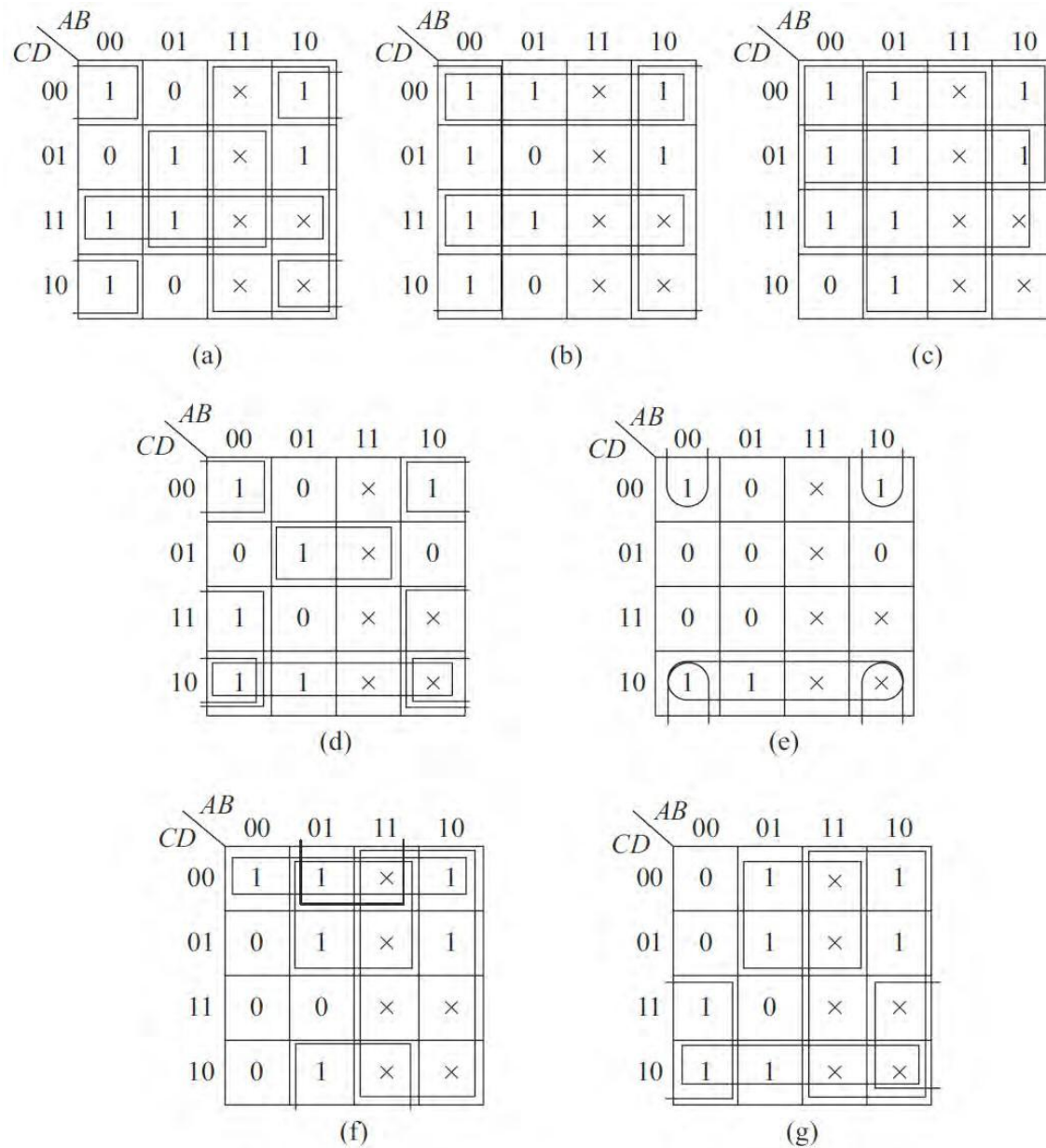


Fig. 5.25 *K-maps of Table 5.15*

$$a = \bar{B}\bar{D} + BD + CD + A$$

$$b = \bar{B} + \bar{C}\bar{D} + CD$$

$$c = B + \bar{C} + D = \overline{\bar{B}\bar{C}\bar{D}}$$

$$d = \bar{B}\bar{D} + C\bar{D} + \bar{B}C + B\bar{C}D$$

$$e = \bar{B}\bar{D} + C\bar{D}$$

$$f = A + \bar{C}\bar{D} + B\bar{C} + B\bar{D}$$

$$g = A + B\bar{C} + \bar{B}C + C\bar{D}$$


 
 
 
 
 
 


Fig. 5.26 NAND Gate Realisations of Eqs (5.38) to (5.44)

 

## Encoder

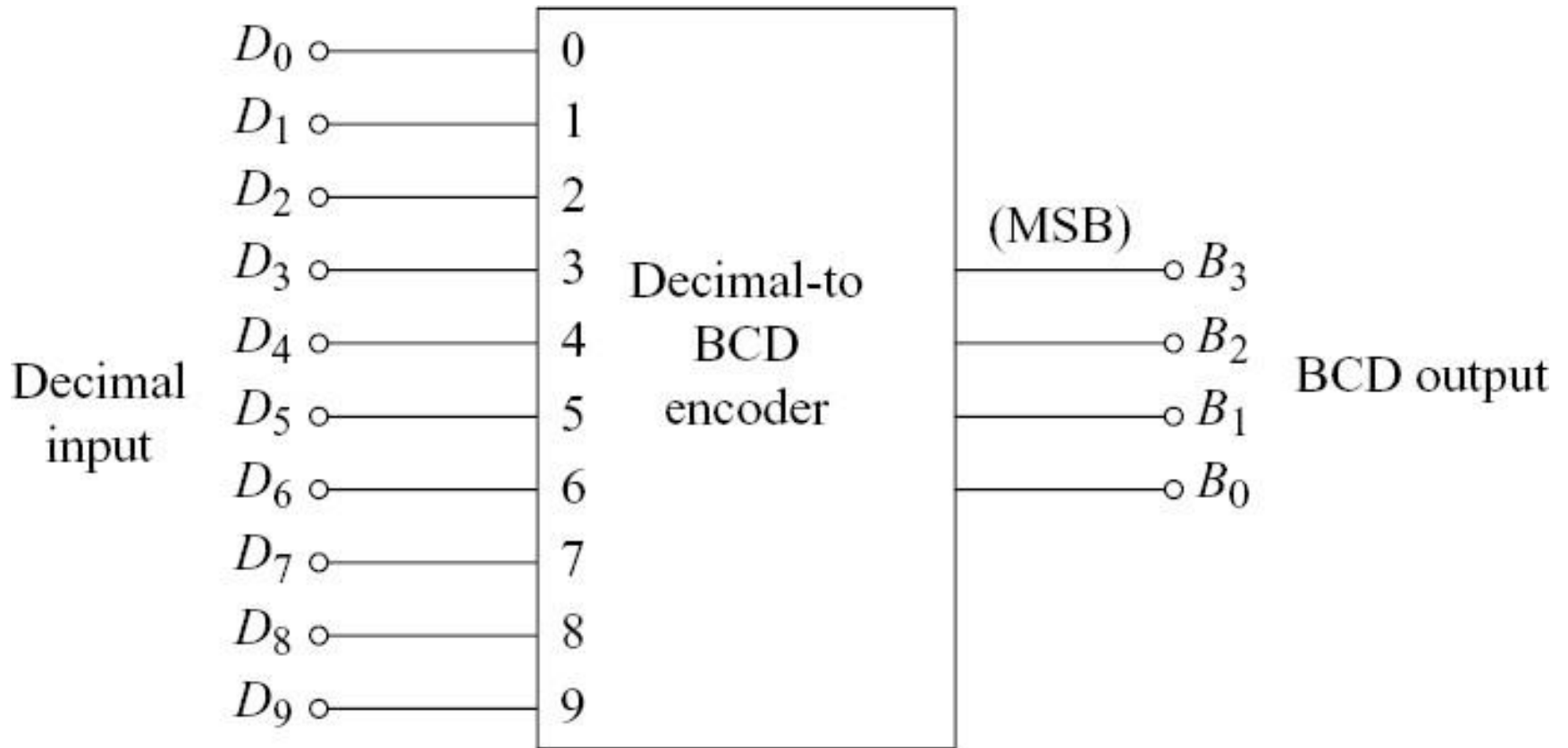


Fig. 5.27      *Block Diagram of Decimal-to-BCD Encoder*

-----

## Truth Table of Decimal-to-BCD Encoder

Input	Output			
Decimal digit	$B_3$	$B_2$	$B_1$	$B_0$
$D_0$	0	0	0	0
$D_1$	0	0	0	1
$D_2$	0	0	1	0
$D_3$	0	0	1	1
$D_4$	0	1	0	0
$D_5$	0	1	0	1
$D_6$	0	1	1	0
$D_7$	0	1	1	1
$D_8$	1	0	0	0
$D_9$	1	0	0	1

From the truth table, we obtain the logic expressions for the outputs.

$$B_3 = D_8 + D_9$$

$$B_2 = D_4 + D_5 + D_6 + D_7$$

$$B_1 = D_2 + D_3 + D_6 + D_7$$

$$B_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

## Multiplexer

 


Fig. 5.29 *Block Diagram of a 4:1 Multiplexer*

-----

 


Fig. 5.28 *Implementation of Decimal-to-BCD Encoder*

-----

## Truth Table of a 4:1 Multiplexer

Select input		Output
$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

$$Y = \bar{S}_0 \cdot \bar{S}_1 \cdot I_0 + S_0 \cdot \bar{S}_1 \cdot I_1 + \bar{S}_0 \cdot S_1 \cdot I_2 + S_0 \cdot S_1 \cdot I_3$$

Its realisation using NAND gates and inverters is shown in Fig.5.30.

 



Fig. 5.30

## Decimal-to-Binary Conversion

### Example 2.4

Convert  $(13)_{10}$  to an equivalent base-2 number.

*Solution*

 

Thus,  $(13)_{10} = (1101)_2$

### Example 2.5

Convert  $(0.65625)_{10}$  to an equivalent base-2 number.

*Solution*

$\begin{array}{r} 0.65625 \\ \times 2 \\ \hline 1.31250 \end{array}$	$\rightarrow$	$\begin{array}{r} 0.31250 \\ \times 2 \\ \hline 0.62500 \end{array}$	$\rightarrow$	$\begin{array}{r} 0.62500 \\ \times 2 \\ \hline 1.25000 \end{array}$	$\rightarrow$	$\begin{array}{r} 0.25000 \\ \times 2 \\ \hline 0.50000 \end{array}$	$\rightarrow$	$\begin{array}{r} 0.50000 \\ \times 2 \\ \hline 1.00000 \end{array}$
$\downarrow$		$\downarrow$		$\downarrow$		$\downarrow$		$\downarrow$
1		0		1		0		1

Thus,  $(0.65625)_{10} = (0.10101)_2$


## Example 2.6

Express the following decimal numbers in the binary form:

(a) 25.5 (b) 10.625 (c) 0.6875

### *Solution*

(a) *Integer part*

 

Therefore,  $(25)_{10} = (11001)_2$

*Fractional part*

$$\begin{array}{r} 0.5 \\ \times 2 \\ \hline 1.0 \\ \downarrow \\ 1 \end{array}$$

i.e.,  $(0.5)_{10} = (0.1)_2$

Therefore,  $(25.5)_{10} = (11001.1)_2$

(b) *Integer part*  $(10)_{10} = (1010)_2$

*Fractional part*

$$\begin{array}{ccc} \begin{array}{r} 0.625 \\ \times 2 \\ \hline 1.250 \\ \downarrow \\ 1 \end{array} & \xrightarrow{\quad} & \begin{array}{r} 0.250 \\ \times 2 \\ \hline 0.500 \\ \downarrow \\ 0 \end{array} & \xrightarrow{\quad} & \begin{array}{r} 0.500 \\ \times 2 \\ \hline 1.000 \\ \downarrow \\ 1 \end{array} \end{array}$$

i.e.,  $(0.625)_{10} = (0.101)_2$

Therefore,  $(10.625)_{10} = (1010.101)_2$



(c)

$0.6875$	$\rightarrow$	$0.3750$	$\rightarrow$	$0.7500$	$\rightarrow$	$0.5000$
$\times 2$		$\times 2$		$\times 2$		$\times 2$
$\hline 1.3750$		$\hline 0.7500$		$\hline 1.5000$		$\hline 1.0000$
$\downarrow$		$\downarrow$		$\downarrow$		$\downarrow$
1		0		1		1

Therefore,  $(0.6875)_{10} = (0.1011)_2$

# BINARY ARITHMETIC

Arithmetic operations such as addition, subtraction, multiplication, and division are Performed similar to decimal arithmetic.

## Binary Addition

### Rules of Binary Addition

Augend	Addend	Sum	Carry	Result
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	0	1	10

### Example 2.13

Add the binary numbers:

(i) 1011 and 1100      (ii) 0101 and 1111

*Solution*

			(1)	(1)	(1)	← carry
(i)		1	0	1	1	
	(+)	1	1	0	0	
		1	0	1	1	
		↑				carry

(ii)		0	1	0	
	(+)	1	1	1	
		1	0	1	0
		↑			
		carry			

# Binary Subtraction

## Rules of Binary Subtraction

Minuend	Subtrahend	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

### Example 2.15

Perform the following subtraction:

$$\begin{array}{r} 1011 \\ - 0110 \\ \hline \end{array}$$

*Solution*



Here, in columns 1 and 2, borrow = 0 and in column 3 it is 1. Therefore, in column 4 first subtract 0 from 1 and from this result obtained subtract the borrow bit.

# Binary Multiplication

Binary multiplication is similar to decimal multiplication.

## Example 2.16

Multiply 1001 by 1101.

*Solution*

1 0 0 1		Multiplicand
× 1 1 0 1		Multiplier
-----		
1 0 0 1	I	Partial Products
0 0 0 0	II	
1 0 0 1	III	
1 0 0 1	IV	
-----		
1 1 1 0 1 0 1		Final Product

In a digital circuit, the multiplication operation is performed by repeated additions of all partial products to obtain the final product.

## Binary Division

Binary division is obtained using the same procedure as decimal division.

### Example 2.17

Divide 1 1 1 0 1 0 1 by 1 0 0 1.

*Solution*

$$\begin{array}{r} \text{Divisor} \rightarrow 1001 \overline{) 1110101} \\ \underline{1001} \phantom{000000} \\ 1011 \phantom{000000} \\ \underline{1001} \phantom{000000} \\ 001001 \phantom{000000} \\ \underline{1001} \phantom{000000} \\ 0000 \phantom{000000} \end{array}$$

← Quotient  
← Dividend

Ans: 1101

## OCTAL NUMBER SYSTEM

The Number system with base(or radix) eight is known as the octal number system.

### Octal-to-Decimal Conversion

#### Example 2.20

Convert  $(6327.4051)_8$  into its equivalent decimal number.

#### *Solution*

Using the weights given in Table 2.1, we obtain

$$\begin{aligned}(6327.4051)_8 &= 6 \times 8^3 + 3 \times 8^2 + 2 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1} \\ &\quad + 0 \times 8^{-2} + 5 \times 8^{-3} + 1 \times 8^{-4} \\ &= 3072 + 192 + 16 + 7 + \frac{4}{8} + 0 + \frac{5}{512} + \frac{1}{4096} \\ &= (3287.5100098)_{10}\end{aligned}$$

Thus,  $(6327.4051)_8 = (3287.5100098)_{10}$

# Decimal-to-Octal Conversion

## Example 2.21

- (a) Convert  $(247)_{10}$  into octal
- (b) Convert  $(0.6875)_{10}$  into octal
- (c) Convert  $(3287.5100098)_{10}$  into octal

### Solution

(a)

	Quotient	Remainder
$\begin{array}{r} 247 \\ \hline 8 \end{array}$	30	7
$\begin{array}{r} 30 \\ \hline 8 \end{array}$	3	6
$\begin{array}{r} 3 \\ \hline 8 \end{array}$	0	3

Arrows indicate the flow of remainders from bottom to top: 3, 6, 7.

Thus,  $(247)_{10} = (367)_8$

(b)

$\begin{array}{r} 0.6875 \\ \times 8 \\ \hline 5.5000 \\ \downarrow \\ 5 \end{array}$	$\begin{array}{r} 0.5000 \\ \times 8 \\ \hline 4.0000 \\ \downarrow \\ 4 \end{array}$
---	---

A curved arrow connects the 5.5000 result to the 0.5000 input of the second step.

Thus,  $(0.6875)_{10} = (0.54)_8$

(c) *Integer part:*

	Quotient
3287/8	410
410/8	51
51/8	6
6/8	0

Remainder

7				
2				
3				
6				
	6	3	2	7

Thus,  $(3287)_{10} = (6327)_8$

*Fractional part:*

0.5100098	0.0800784	0.6406272	0.1250176
$\times 8$	$\times 8$	$\times 8$	$\times 8$
4.0800784	0.6406272	5.1250176	1.0001408
↓	↓	↓	↓
4	0	5	1

Thus  $(0.5100098)_{10} \approx (0.4051)_8$

Therefore,  $(3287.5100098)_{10} = (6327.4051)_8$



# Octal-to-Binary Conversion

## Binary and Decimal Equivalents of Octal Numbers

Octal	Decimal	Binary
0	0	000
1	1	001
2	2	010
3	3	011
4	4	100
5	5	101
6	6	110
7	7	111
10	8	001000
11	9	001001
12	10	001010
13	11	001011
14	12	001100
15	13	001101
16	14	001110
17	15	001111

# Binary-to-Octal Conversion

## Example 2.25

Convert the following binary numbers to octal numbers

- (a) 11001110001.000101111001
- (b) 1011011110.11001010011
- (c) 111110001.10011001101

### *Solution*

- (a) 011 001 110 001.000 101 111 001 =  $(3161.0571)_8$
- (b) 001 011 011 110.110 010 100 110 =  $(1336.6246)_8$
- (c) 111 110 001.100 110 011 010 =  $(761.4632)_8$

# HEXADECIMAL NUMBER SYSTEM

The Number System with base (or radix) 16 is known as hexadecimal number system.

## Binary and Decimal Equivalents of Hexadecimal Numbers

Hexadecimal	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

## Hexadecimal-to-Decimal Conversion

### Example 2.28

Obtain decimal equivalent of hexadecimal number  $(3A.2F)_{16}$

#### *Solution*

Using Eq. (2.1),

$$\begin{aligned}(3A.2F)_{16} &= 3 \times 16^1 + 10 \times 16^0 + 2 \times 16^{-1} + 15 \times 16^{-2} \\ &= 48 + 10 + \frac{2}{16} + \frac{15}{16^2} \\ &= (58.1836)_{10}\end{aligned}$$

# Decimal-to-Hexadecimal Conversion


## Example 2.29

Convert the following decimal numbers into hexadecimal numbers.

(a) 95.5    (b) 675.625

### *Solution*

(a) *Integer part*

 

Thus,  $(95)_{10} = (5F)_{16}$

*Fractional part*

$$\begin{array}{r} 0.5 \\ \times 16 \\ \hline 8.0 \\ \downarrow \\ 8 \end{array}$$

Thus,  $(0.5)_{10} = (0.8)_{16}$

Therefore,  $(95.5)_{10} = (5F.8)_{16}$

(b) *Integer part*

	Quotient
$675/16$	42
$42/16$	2
$2/16$	0

Remainder
3
10
2
2
A
3

Thus,  $(675)_{10} = (2A3)_{16}$

*Fractional part*

$$\begin{array}{r} 0.625 \\ \times 16 \\ \hline 10.000 \\ \downarrow \\ A \end{array}$$

Thus,  $(0.625)_{10} = (0.A)_{16}$

Therefore,  $(675.625)_{10} = (2A3.A)_{16}$

## Hexadecimal-to-Binary Conversion

### Example 2.30

Convert  $(2F9A)_{16}$  to equivalent binary number.

#### *Solution*

Using Table 2.7, find the binary equivalent of each hex digit.

$$\begin{aligned}(2F9A)_{16} &= (0010\ 1111\ 1001\ 1010)_2 \\ &= (0010111110011010)_2\end{aligned}$$

## Binary-to-Hexadecimal Conversion

### Example 2.31

Convert the following binary numbers to their equivalent hex numbers.

(a) 10100110101111

(b) 0.00011110101101

### *Solution*

$$(a) \quad (10100110101111)_2 = \underbrace{0010}_2 \underbrace{1001}_9 \underbrace{1010}_A \underbrace{1111}_F$$

$$\therefore (10100110101111)_2 = (29AF)_{16}$$

$$(b) \quad (0.00011110101101)_2 = \underbrace{0.0001}_1 \underbrace{1110}_E \underbrace{1011}_B \underbrace{0100}_4$$

$$\therefore (0.00011110101101)_2 = (0.1EB4)_{16}$$