

FLIP-FLOPs

 


Fig. 7.1 *Block Diagram of a Sequential Circuit*

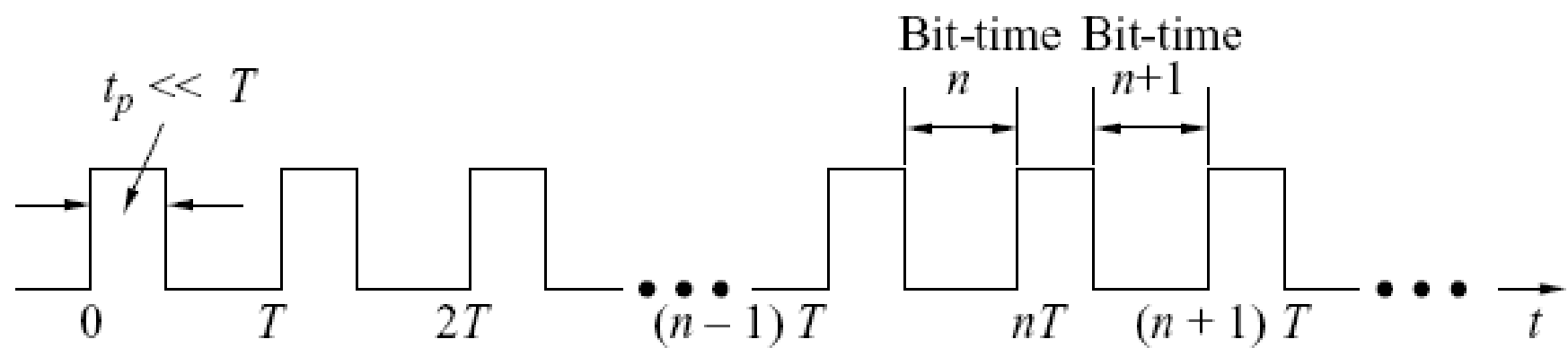


Fig. 7.2 *A Train of Pulses*

A 1-BIT MEMORY CELL

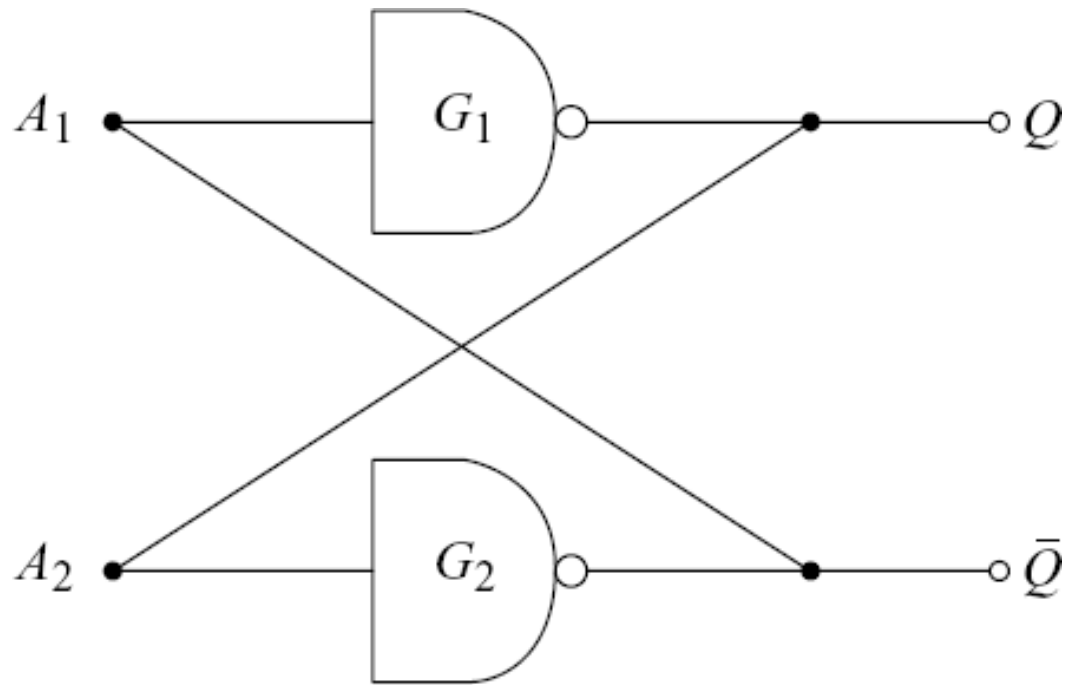


Fig. 7.3

*Cross-coupled Inverters as a
Memory Element*

 


Fig. 7.4

The Memory Cell with Provision for Entering Data

CLOCKED S-R FLIP-FLOP

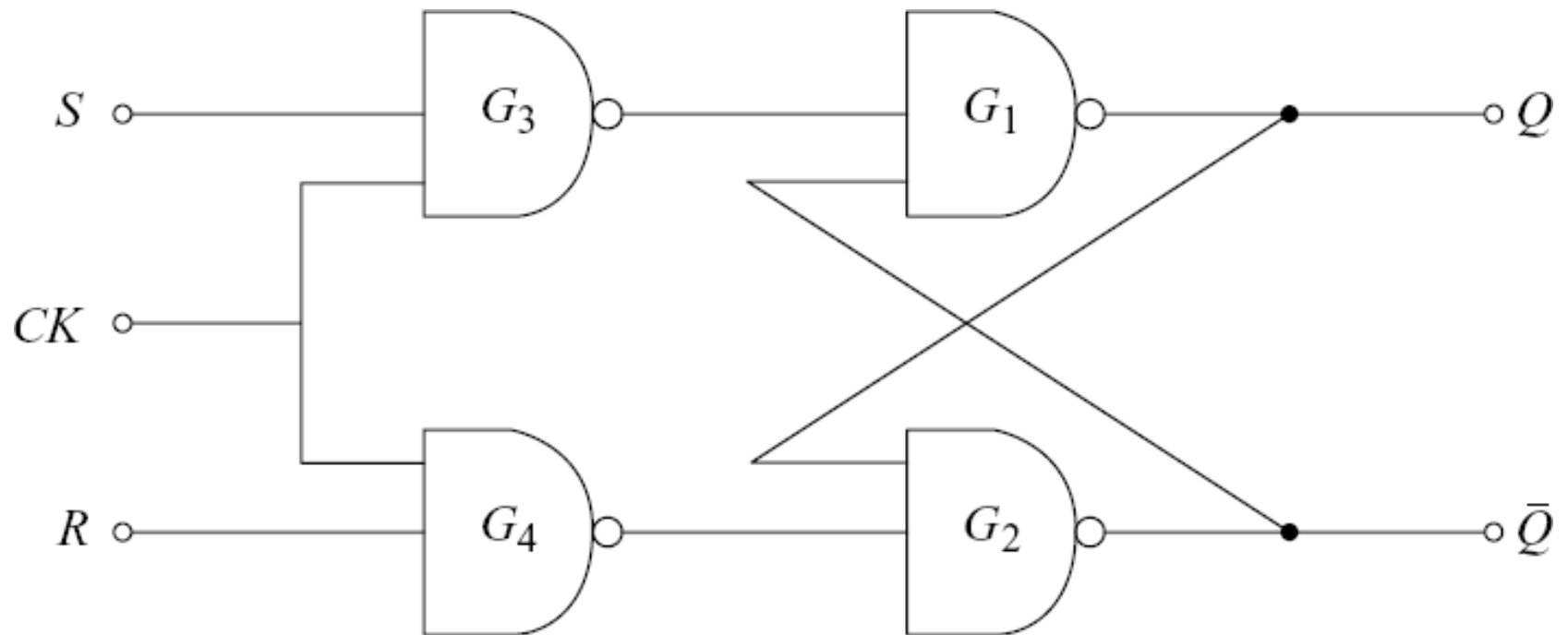


Fig. 7.5 *A Clocked S-R FLIP-FLOP*

Table 7.1 *Truth Table of S–R FLIP–FLOP*

Inputs		Output Q_{n+1}
S_n	R_n	
0	0	Q_n
1	0	1
0	1	0
1	1	?

 


Fig. 7.6 *Logic Symbol of Clocked S–R*
FLIP–FLOP

 


Fig. 7.7 (a) An S-R FLIP-FLOP with Preset and Clear,
 - - - - - (b) Its Logic Symbol

 


Fig. 7.7 (Continued)

Table 7.2 *Summary of Operation of S-R FLIP-FLOP*

Inputs			Output Q	Operation performed
CK	Cr	Pr		
1	1	1	Q_{n+1} (Table 7.1)	Normal FLIP-FLOP
0	0	1	0	Clear
0	1	0	1	Preset

J-K FLIP-FLOP

 


Fig. 7.8 *An S-R FLIP-FLOP Converted into J-K FLIP-FLOP*

Table 7.3a *Truth Table for Fig. 7.8*

Data inputs		Outputs		Inputs to S–R FF		Output
J_n	K_n	Q_n	$\overline{Q}_n$	S_n	R_n	
0	0	0	1	0	0	$0 \Big = Q_n$ $1 \Big $
0	0	1	0	0	0	
1	0	0	1	1	0	$1 \Big = 1$ $1 \Big $
1	0	1	0	0	0	
0	1	0	1	0	0	$0 \Big = 0$ $0 \Big $
0	1	1	0	0	1	
1	1	0	1	1	0	$1 \Big = \overline{Q}_n$ $0 \Big $
1	1	1	0	0	1	

Table 7.3b *Truth Table of J–K FLIP–FLOP*

Inputs		Output
J_n	K_n	
0	0	Q_n
1	0	1
0	1	0
1	1	$\overline{Q}_n$

 


Fig. 7.9 *A J-K FLIP-FLOP Using NAND Gates*

 


Fig. 7.10 *Logic Symbols of J-K FLIP-FLOP*

The Master-Slave J - K FLIP-FLOP

 


Fig. 7.12 A Master-Slave J - K FLIP-FLOP

 


Fig. 7.13

*A Master-Slave J-K FLIP-FLOP
Logic Symbol*

D-TYPE FLIP-FLOP

 


Fig. 7.14 (a) A J-K or S-R FLIP-FLOP Converted into a D-type FLIP-FLOP (b) its Logic Symbol

Table 7.4 Truth Table of a D-type FLIP-FLOP

Input D_n	Output Q_{n+1}
0	0
1	1

T-TYPE FLIP-FLOP

 


Fig. 7.15 (a) A J-K FLIP-FLOP Converted into a T-type FLIP-FLOP (b) its Logic Symbol

Table 7.5 Truth Table of T-type FLIP-FLOP

Input	Output
T_n	Q_{n+1}
0	Q_n
1	$\bar{Q}_n$

 


Fig. 7.16

An S-R FLIP-FLOP as a Toggle Switch

EXCITATION TABLE OF FLIP-FLOP

Table 7.6 *Excitation Table of FLIP-FLOPs*

Present State	Next State	<i>S-R</i>	<i>FF</i>	<i>J-K</i>	<i>FF</i>	<i>T-FF</i>	<i>D-FF</i>
		<i>S_n</i>	<i>R_n</i>	<i>J_n</i>	<i>K_n</i>	<i>T_n</i>	<i>D_n</i>
0	0	0	×	0	×	0	0
0	1	1	0	1	×	1	1
1	0	0	1	×	1	1	0
1	1	×	0	×	0	0	1

CLOCKED FLIP-FLOP DESIGN

 


Fig. 7.17 *The General Model of the FLIP-FLOP*

Conversion from One Type of FLIP-FLOP to Another Type

 


Fig. 7.19

The General Model Used to Convert One Type of FLIP-FLOP to Another Type

EDGE-TRIGGERED FLIP-FLOPS

Set-up time (t_s)


Hold time (t_h)

Propagation Delays

Clock Pulse Width

Preset and Clear Pulse Width

Maximum Clock Frequency

 

(a)

 


Fig. 7.21 FLIP-FLOP Timings (a) Set-up and Hold Timings (b) Propagation Delays (c) Clock LOW and HIGH Timings

Timing Parameters of TTL and CMOS FLIP-FLOPs

Parameter	TTL			CMOS			UNIT
	74LS74A	74LS112	74F74	74HC74A	74HC112	74AHC74	
t_s (set up time)	20	20	2	14	25	5	ns
t_h (hold time)	5	0	1	3	0	0.5	ns
t_{pHL} (CK to Q)	40	24	6.8	17	31	4.6	ns
t_{pLH} (CK to Q)	25	16	8	17	31	4.6	ns
t_{pHL} (Cr to Q)	40	24	9	18	41	4.8	ns
t_{pLH} (Pr to Q)	25	16	6.1	18	41	4.8	ns
t_{CH} (clock HIGH time)	25	20	4	10	25	5	ns
t_{CL} (clock LOW time)	25	15	5	10	25	5	ns
t_{WL} (Pr or Cr LOW time)	25	15	4	10	25	5	ns
f_{MAX} (Max. frequency)	25	30	100	35	20	170	MHz

APPLICATIONS OF FLIP-FLOPs

1. Bounce elimination switch,
2. Latch,
3. Registers,
4. Counters,
5. Memory, etc.

Bounce-Elimination Switch

Example 7.4

Show that the circuit of Fig. 7.23*a* acts as a bounce-elimination (chatterless) switch.


Solution

The waveforms at $\bar{S}$, $\bar{R}$, Q , and $\bar{Q}$ are illustrated in Fig. 7.23*b*. The switch (SW) is thrown from position *A* to *B* at $t = 0$. Therefore, at $t = 0^+$ the voltage at $\bar{S}$ will be V_{CC} (logic 1) and will continue to remain so as long as the switch is not thrown to position *A* again.

At $\bar{R}$ (B), the voltage at $t = 0^-$ is V_{cc} (logic 1) and goes to 0 V (logic 0) at t_1 (t_1 being the time delay of the switch). The switch arm makes contact at B at $t = t_1$, and then bounces off. Therefore, the level at $\bar{R}$ changes from 0 to 1 and vice-versa. This is illustrated in Fig. 7.23b.

Between $t = 0$ and $t = t_1$, both the inputs $\bar{S}$ and $\bar{R}$ are at logic 1 and therefore, Q does not change. The output Q changes at t_1 and becomes 0. Now, even when $\bar{R}$ is changing at t_2, t_3 , etc. Q does not change. This shows that it is a chatterless switch.

 The latch used in Fig. 7.23a can be replaced by the IC 74279 which is a quad $\bar{S} - \bar{R}$ latch.



(a) Latch

 


Fig. 7.23 (a) A Bounce-Elimination Switch (b) Waveforms of $\bar{S}$, $\bar{R}$, Q , and $\bar{Q}$

Registers

 


Fig. 7.24 *A 3-bit Register Using FLIP-FLOPS*

Counters

 


Fig. 7.25

A 3-bit Counter Using FLIP-FLOPs

 


Fig. 7.26

Waveforms of Counter of Fig. 7.25

Random-Access Memory

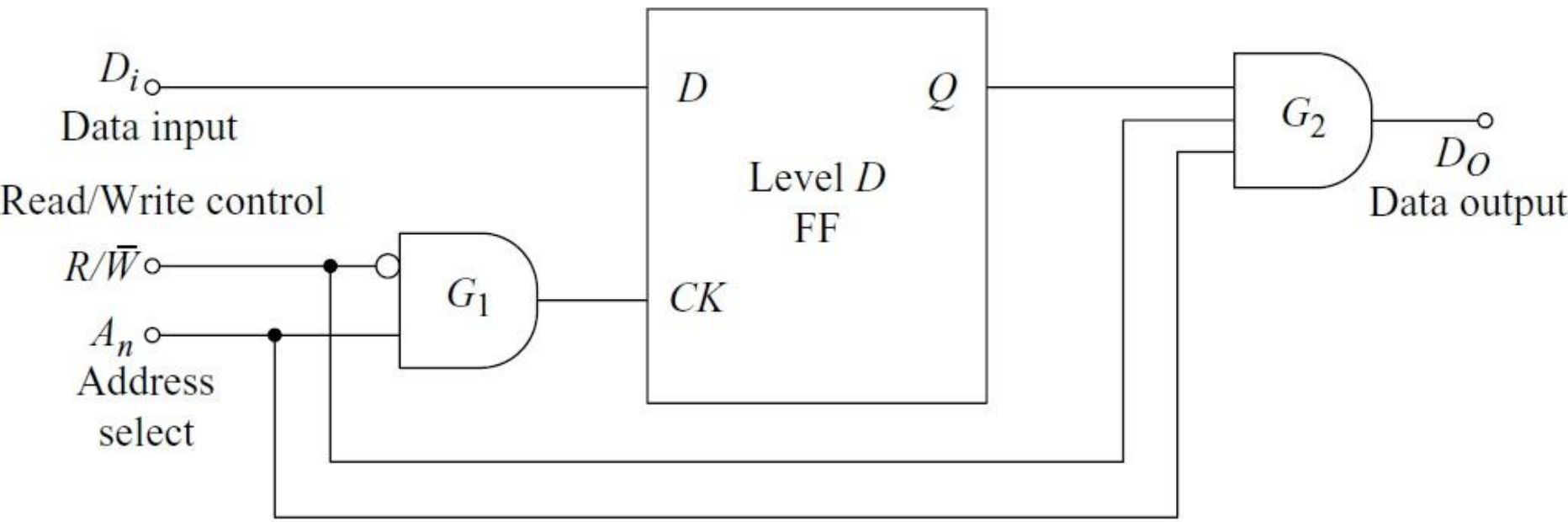


Fig. 7.27 *A 1-bit Read/Write Memory Cell*

Table 7.10 *Function Table of 1-bit Memory Cell*

Inputs			Mode
A_n	$R/\overline{W}$	D_i	
0	×	×	Hold, $D_0 = 0$
1	0	0	Write 0 into memory, $D_0 = 0$
1	0	1	Write 1 into memory, $D_0 = 0$
1	1	×	Read, $D_0 =$ stored D_i bit.